

## Assignment-2

### Problem-1:

When a voltage  $V = 5\text{ V}$  is applied between terminals  $a$  and  $b$  of a linear two-terminal circuit 'X', the circuit draws a current  $I = 2\text{ A}$  as shown in Figure 1 below. When the terminals are shorted,  $3\text{ A}$  current flows as shown in Figure 2.

- (a) Derive a relationship between  $I$  and  $V$ .
- (b) Draw the relationship found in (a).
- (c) If the circuit in Figure 3 is an alternative version of the circuit 'X', determine the voltage  $V'$  and the resistance  $R'$ .

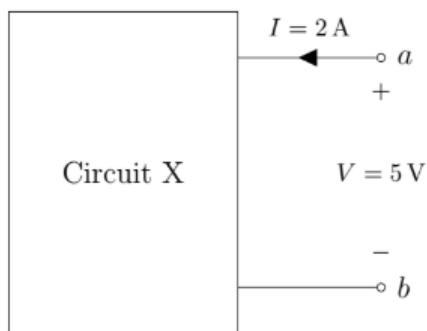


Figure 1

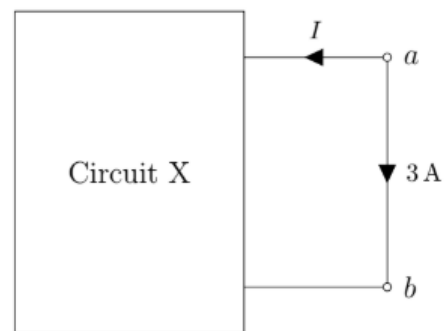


Figure 2


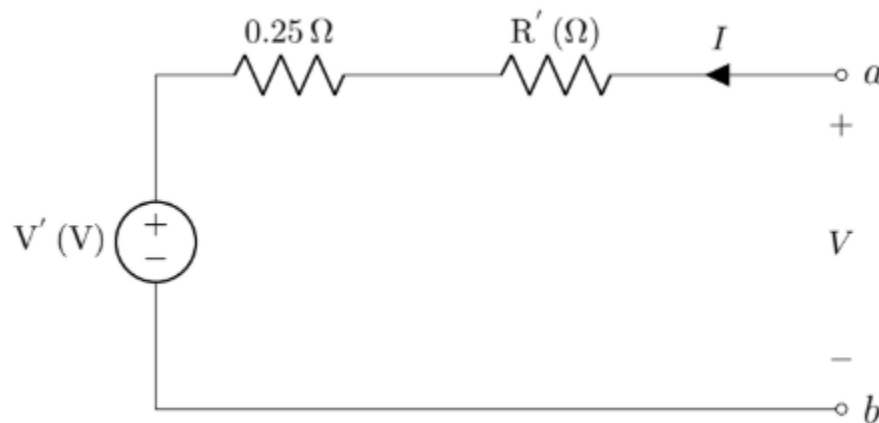


Figure 3
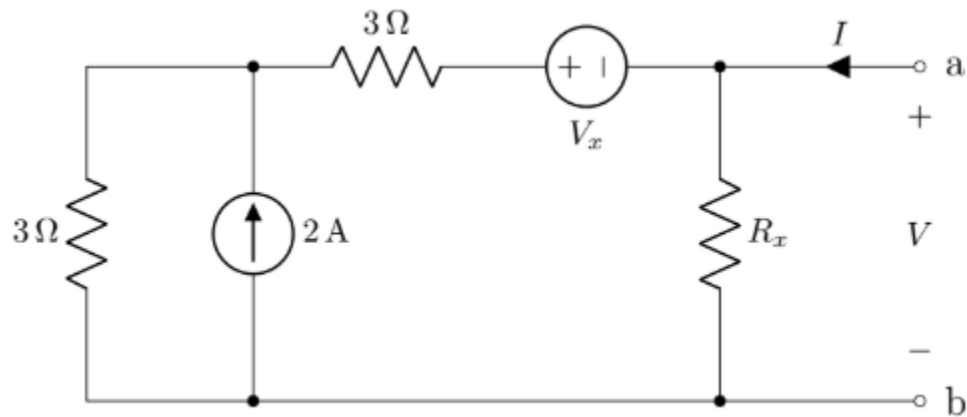
### Problem-2:


In the circuit below, all resistors are practical and cannot have negative values. When a voltage of  $V = 2$  V is applied across terminals a and b, the circuit draws a current of  $I = 3$  A. However, if  $-6$  V is applied, instead of drawing, the circuit supplies 1 A to the terminal a.



- (a) Determine the unknown resistance  $R_x$  in the circuit.
- (b) Find an equivalent representation of the circuit having the minimum number of elements and determine  $V_x$ .
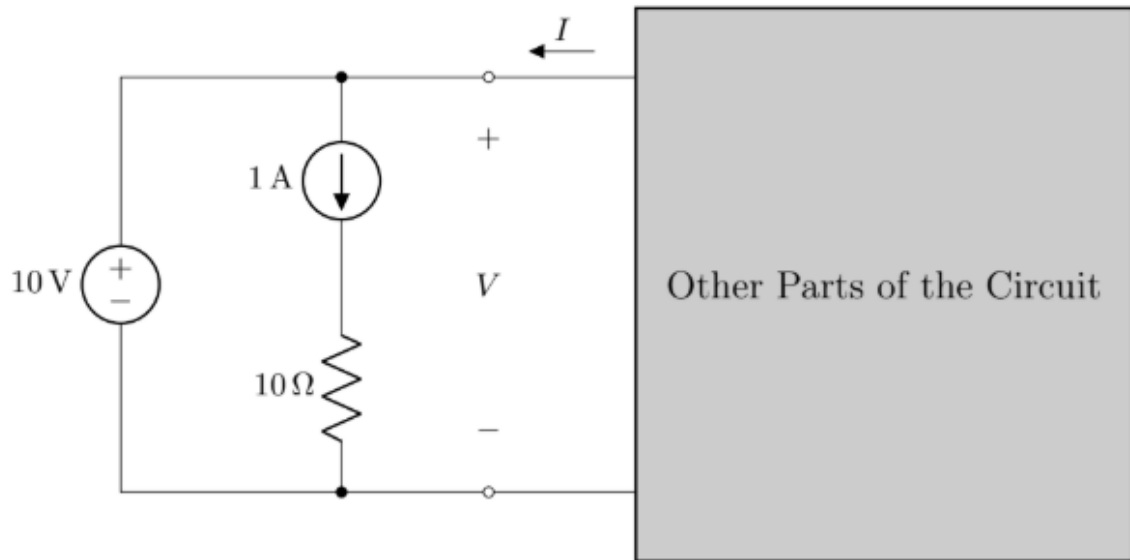
### Problem-3:

You break open your phone charger and find the following circuit. The greyed-out part doesn't contain anything interesting, but the left part of the circuit catches your eye.





(a) (i) Determine  $I - V$  characteristics of the left part of the circuit. i.e. Write an equation that will always hold irrespective of what is inside the greyed-out box.

Hint: The equation cannot have any variables other than  $V$  and/or  $I$ . Everything else should just be a number.

(ii) Based on your answer in (i), plot the  $I - V$  characteristics of the subcircuit.

(b) You notice that the left part of the circuit can actually be replaced with one single equivalent circuit element. Redraw the reduced equivalent circuit.



**Problem-4:**

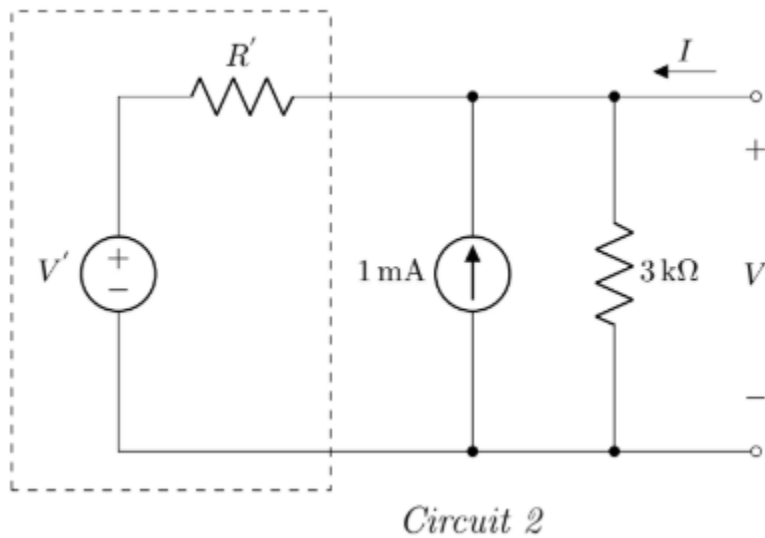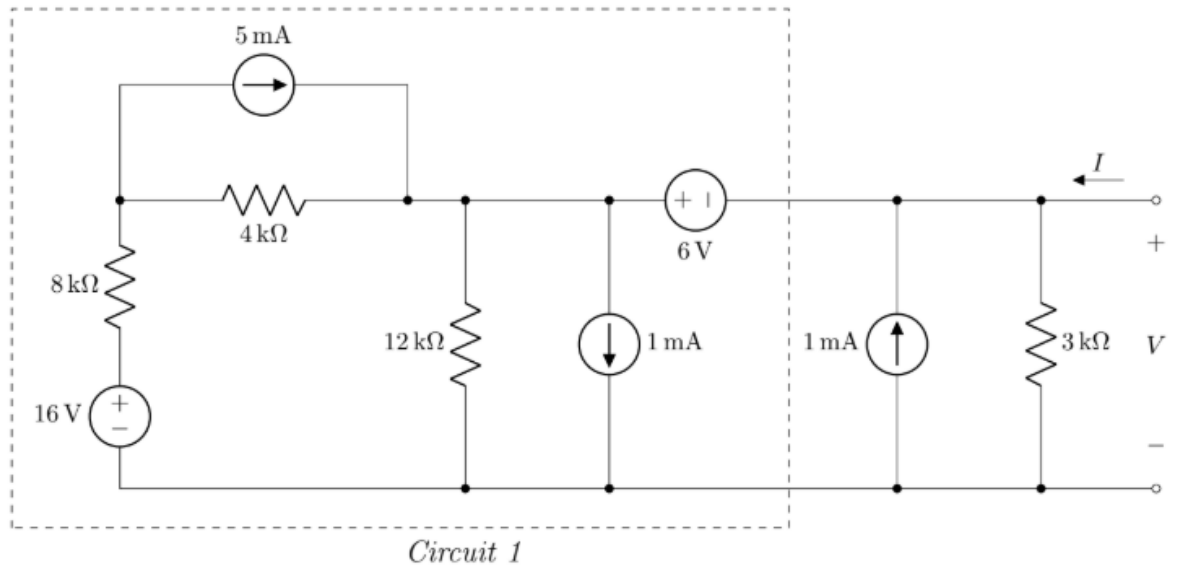

For the circuits shown above,

- (a) Apply Source Transformation to reduce the dashed boxed portion of the Circuit 1 to a single voltage source in series with a resistor as shown in Circuit 2. What are the values of  $V'$  and  $R'$ ?
- (b) Derive a Current-Voltage Relationship from Circuit 2. The  $I - V$  equation cannot contain any variables other than  $I$  and  $V$  pointed out in the diagram. Plot the  $I - V$  relation

**Problem-5:**

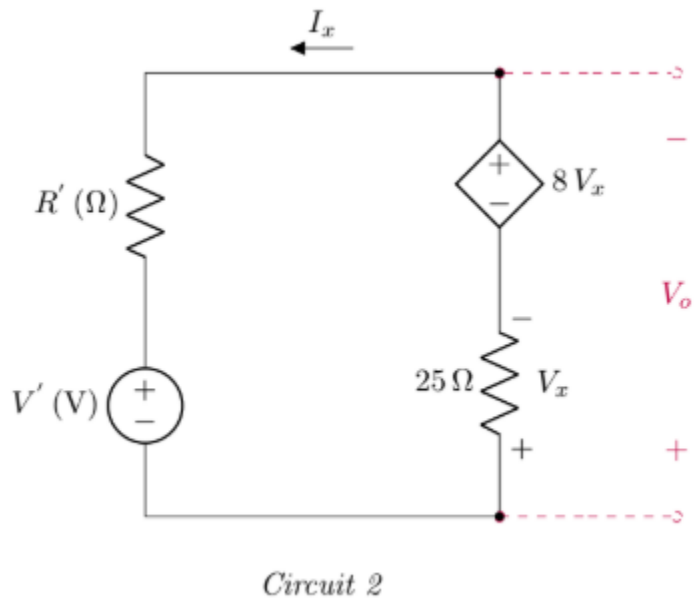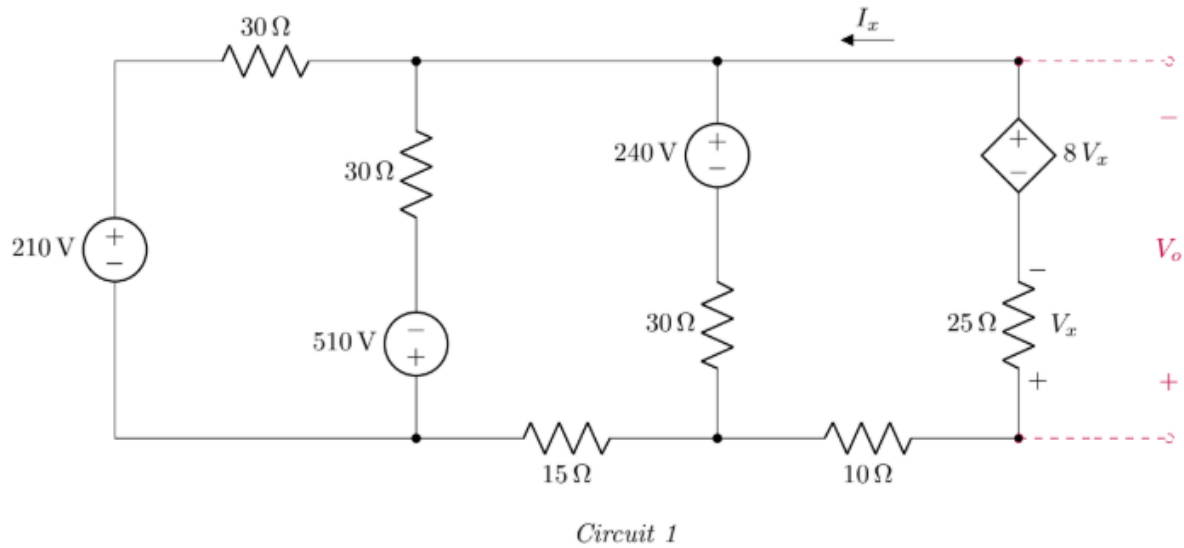


Apply Source Transformation to answer the following queries–

- Reduce the Circuit 1 so that it takes the form of Circuit 2. Determine the values of  $V'$  and  $R'$ .
- Determine the values of  $V_x$  and  $I_x$ .
- Determine the value of  $V_o$ .

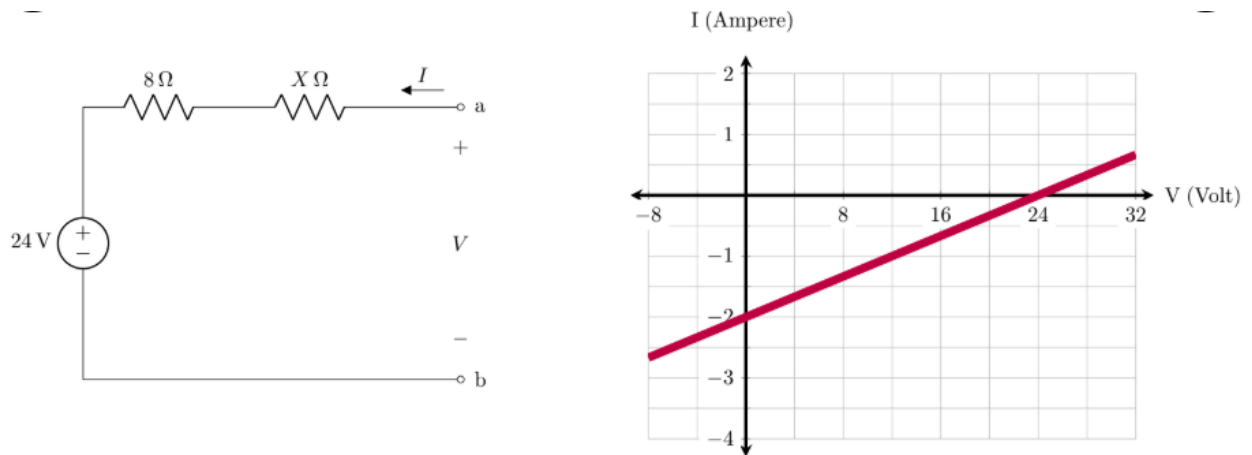
### Problem-6:

For the following circuit, if the  $I$  vs.  $V$  has the relationship shown, determine the value of the unknown resistance  $X$ .



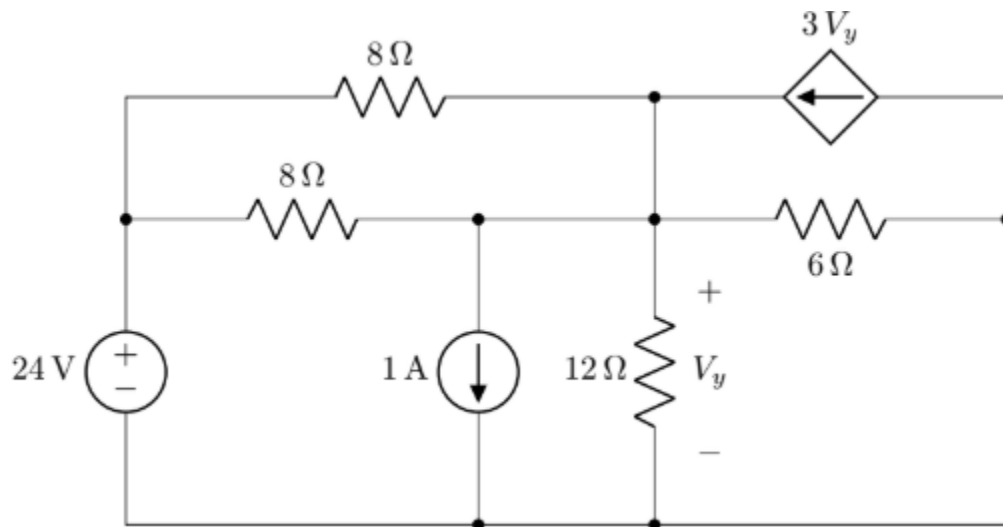
### Problem-7:

Apply Superposition Principle in the following circuit to determine the voltage  $V_y$ .



### Problem-8:

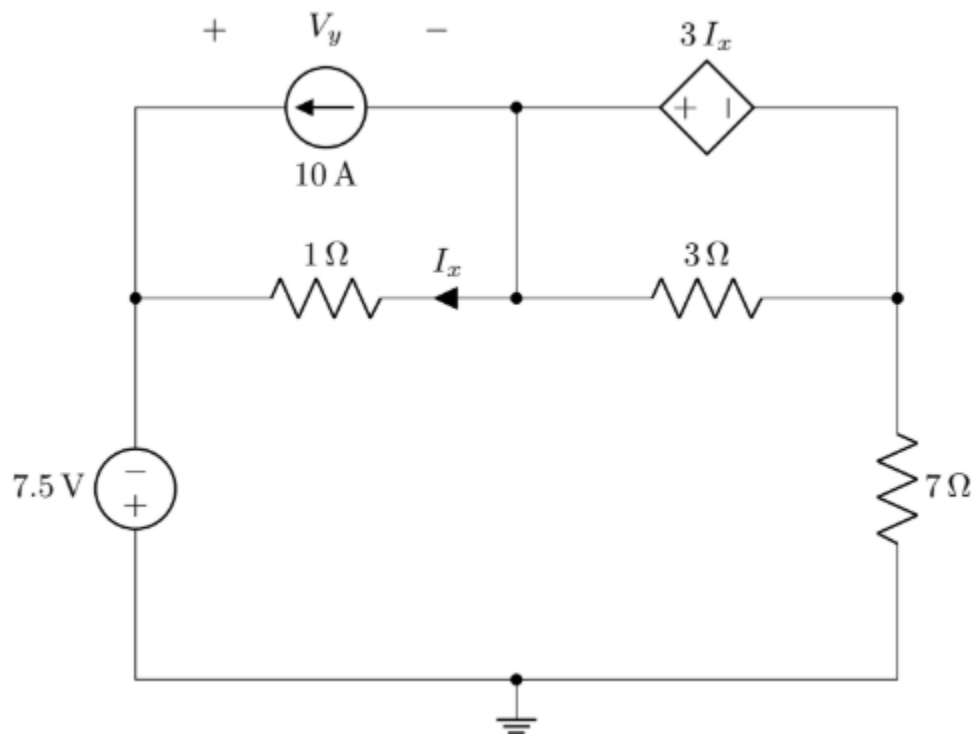


From the above circuit, answer the following questions-

(a) Find  $V_y$  using Superposition principle. After applying Superposition principle you may use any analysis technique you prefer (Nodal, Mesh, Src Tx etc.).

(b) Find the power consumed/supplied by the current source (with proper  $\pm$  sign and unit).

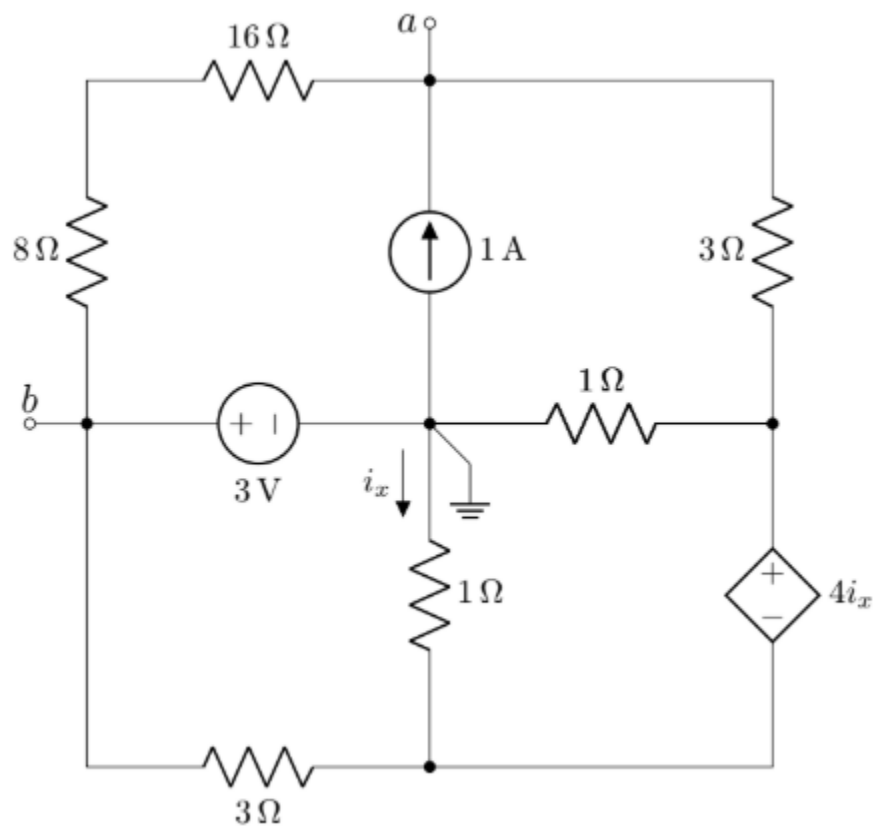**Problem-9:**

Consider the following circuit with open terminals a and b. Currently, no load is connected to the terminals.



Find  $i_x$  using Superposition principle.



**Problem-10:**

Apply Superposition Principle and/or Source Transformation to determine the voltage  $v_y$  in the following circuit.

