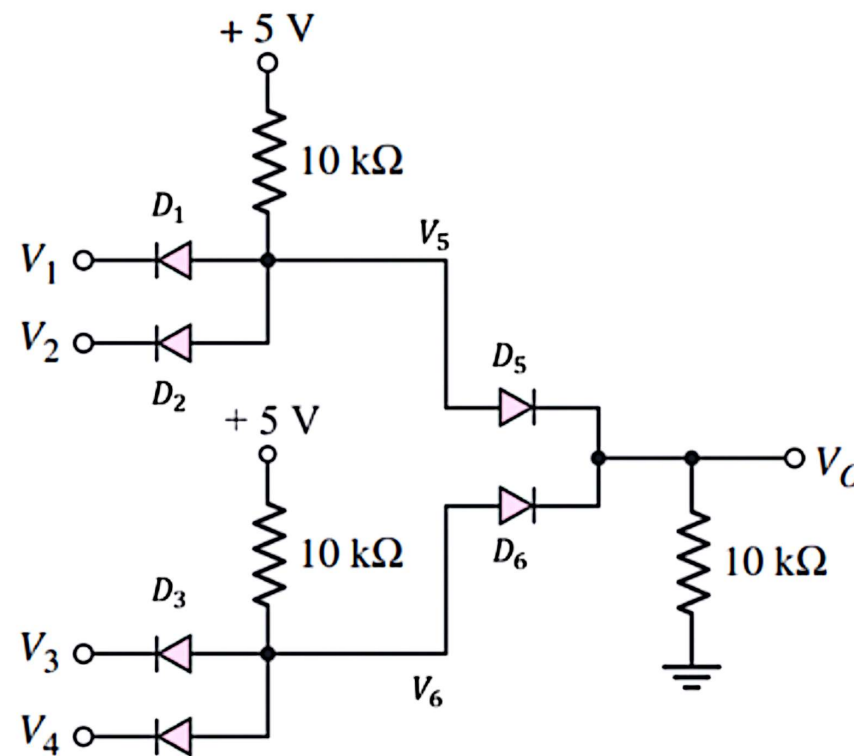


In the adjacent figure we have the following parameters:

$$\begin{aligned} V_{D1} &= 0.3 \text{ V}, & V_1 &= 2 \text{ V} \\ V_{D2} &= 0.5 \text{ V}, & V_2 &= 1.7 \text{ V} \\ V_{D3} &= 0.7 \text{ V}, & V_3 &= 1.5 \text{ V} \\ V_{D4} &= 0.9 \text{ V}, & V_4 &= 1.1 \text{ V} \\ V_{D5} &= V_{D6} &= 1.1 \text{ V} \end{aligned}$$



- Draw the IV characteristics of a diode as per the constant voltage drop + resistance model. Indicate the different operating modes in your graph. **[3]**
- Find V_5 and V_6 . **[3]**
- Find V_O . **[2]**
- Solve the circuit to get V_O , when $V_1=7 \text{ V}$, $V_2 = 8 \text{ V}$ and all other voltages remain the same. (**Hint:** Try to obtain V_5 by solving the portion of the circuit with diodes D_1 and D_2 , by method of assumed states.) **[1 + 1]**



$$i) V_5 = \text{Min}(V_1 + V_{D1}, V_2 + V_{D2}) = \text{Min}(2.3, 2.2) = 2.2 \text{ V}$$

$$V_6 = \text{Min}(V_3 + V_{D3}, V_4 + V_{D4}) = \text{Min}(2.2, 2) = 2 \text{ V}$$

$$ii) V_o = \text{Max}(V_5 - V_{D5}, V_6 - V_{D6}) \\ = \text{Max}(1.1, 0.9) = 1.1 \text{ V}$$

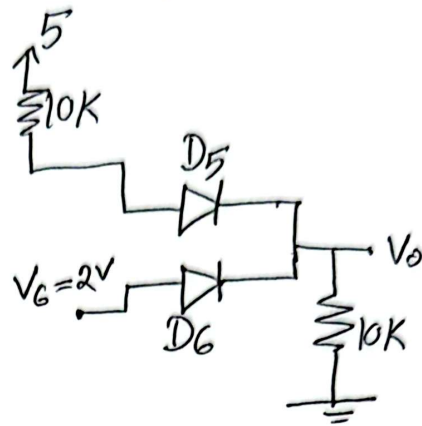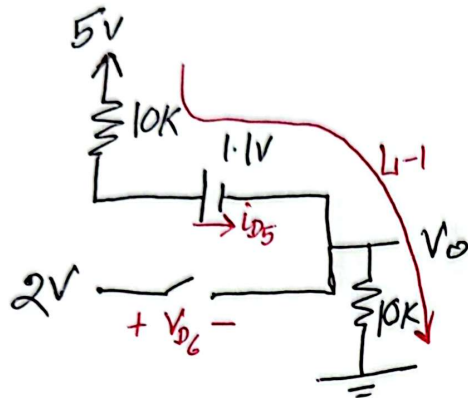iii) For $V_1 = 7V$ & $V_2 = 8V$, D_1 and D_2 are both in reverse bias as both V_1 & V_2 are greater than the $5V$ supply voltage.

Assume $D_5 \rightarrow ON$, $D_6 \rightarrow OFF$



* KVL at L-1

$$5 = 10i_{D5} + 1.1 + 10i_{D5}$$

$$i_{D5} = 0.195 > 0$$

$$V_0 = 0.195 \times 10 = 1.95V$$


$$V_{D6} = 2 - 1.95 = 0.05 < 1.1V$$

Correct Assumption


$$V_0 = 1.95V$$

Q-2 Implement the following expressions using Diodes

i) $f = (A.B) + (C+D)$

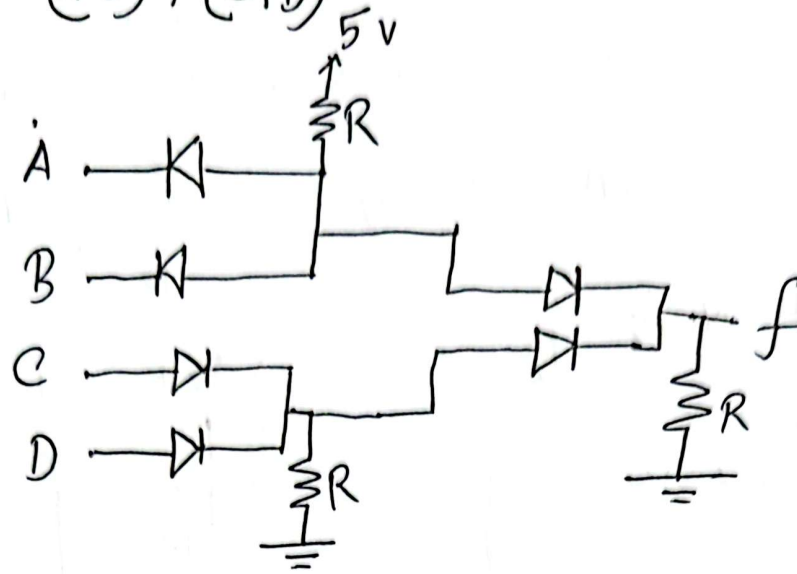

ii) $f = (B.C + D).A$

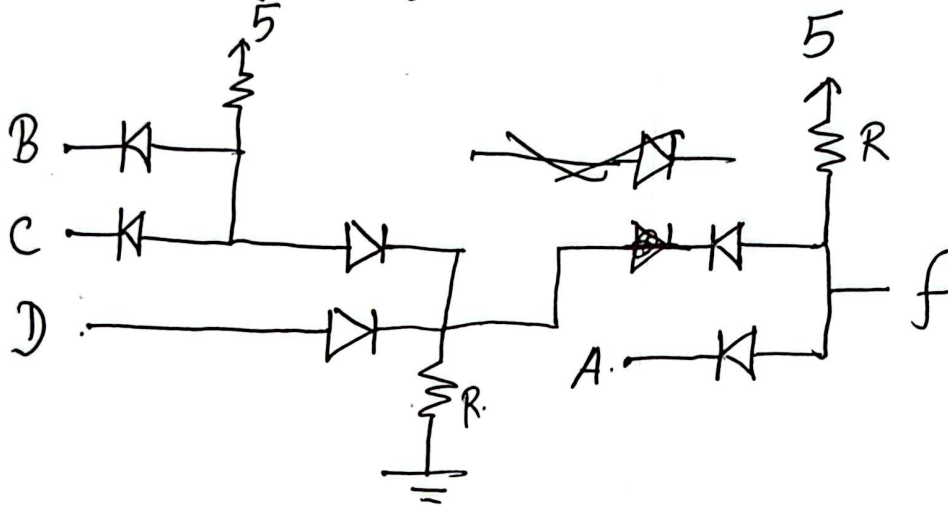

Q-3 Analyze the circuit to calculate

V_x , V_y , I_{D1} & I_{D2} .

Use $V_{D0} = 0.7V$ for both diodes

Assuming D_1 ON & D_2 OFF

KCL at Node V_y

$$I_{D1} = i_1$$

$$\Rightarrow \frac{15 - 0.7 - V_y}{1} = \frac{V_y - 0}{1}$$

$$\Rightarrow V_y = 7.15$$

$$I_{D1} = \frac{15 - 0.7 - 7.15}{1}$$

$$= 7.15 \text{ mA} > 0$$

$$V_{D2} = 0 - V_y = -7.15 < 0.7$$



Assumption is correct

$$V_x - V_y = 0.7$$

$$\Rightarrow V_x = 7.85$$

$$I_{D2} = 0 \text{ mA}$$
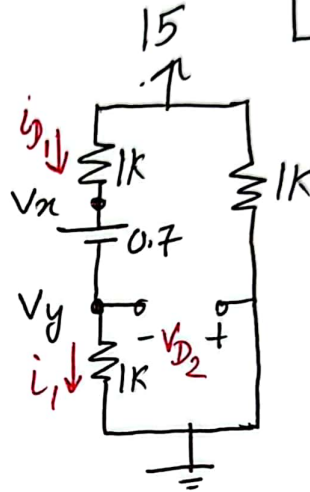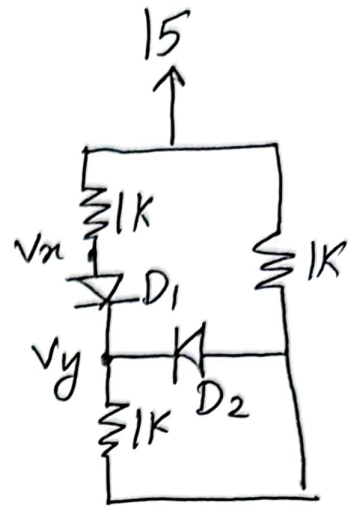
$$\begin{aligned} V_x &= 7.85 \text{ V} \\ V_y &= 7.15 \text{ V} \\ I_{D1} &= 7.15 \text{ mA} \\ I_{D2} &= 0 \text{ mA} \end{aligned}$$



Q-4

Find the current passing through $100k\Omega$ resistor.

$$V_{D0} = 0.7V$$

Assuming D_1 ON, D_2 ON

$$\frac{V_1 - 5}{1.2} + \frac{V_1 - 0}{100} + \frac{V_2 - 5}{1} + \frac{V_2 - 0}{4.7} = 0$$

Format Approach

$$V_1 \left(\frac{1}{1.2} + \frac{1}{100} \right) + V_2 \left(\frac{1}{1} + \frac{1}{4.7} \right) - \frac{5}{1.2} - \frac{5}{1} = 0 \dots (i)$$

$$V_1 - V_2 = 1.4 \dots (ii)$$

$$V_1 = 5.28$$

$$V_2 = 3.88$$



KCL at V_1

$$i_1 + i_2 + i_D = 0$$

$$i_D = -i_1 - i_2 = -\frac{V_1 - 5}{1.2}$$

$$= -0.233 - 0.052$$


$$= -0.285 < 0$$

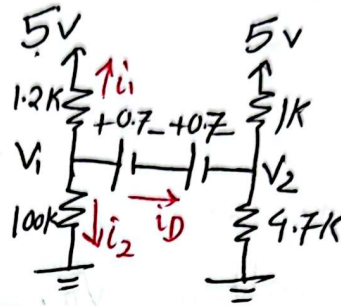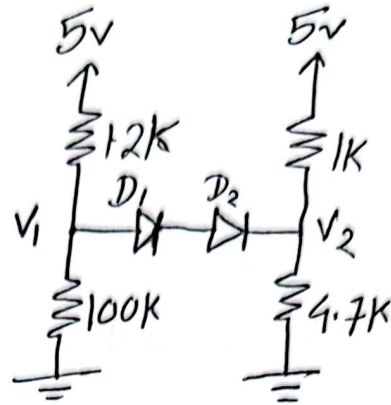

Assumption is wrong


Assuming D_1 & $D_2 \rightarrow \text{Off}$
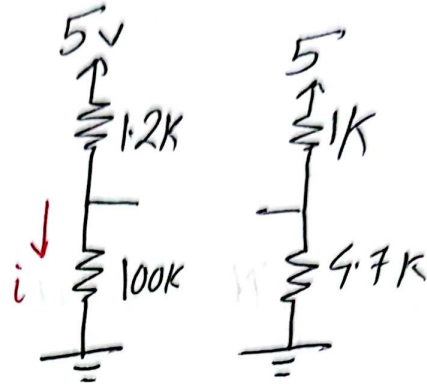
$$\hat{I} = \frac{5}{1.2 + 100} = 0.049 \text{ mA}$$



(85)

Determine the output voltage V_o .

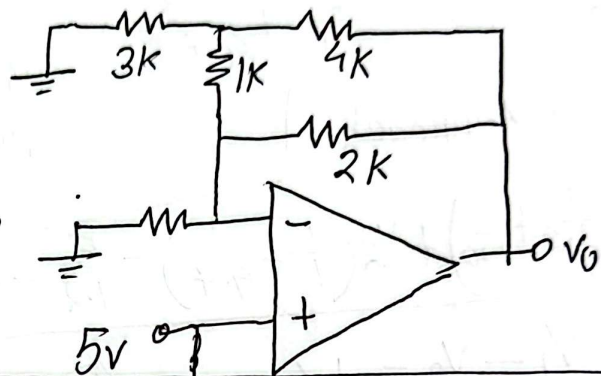

KCL at V_1

$$\begin{aligned} \frac{5-0}{2} + \frac{5-V_o}{2} + \frac{5-V_1}{1} &= 0 \\ \Rightarrow 5 + 5 - V_o + 10 - 2V_1 &= 0 \\ \Rightarrow V_o + 2V_1 &= 20 \dots (i) \end{aligned}$$

KCL at V_1

$$\begin{aligned} \frac{V_1}{3} + \frac{V_1 - V_o}{4} + \frac{V_1 - 5}{1} &= 0 \\ \Rightarrow 4V_1 + 3V_1 - 3V_o + 12V_1 - 60 &= 0 \\ \Rightarrow -3V_o + 19V_1 &= 60 \dots (ii) \end{aligned}$$

Solving eqn (i) & (ii)

$$V_o = 10.4 \text{ V}$$

