
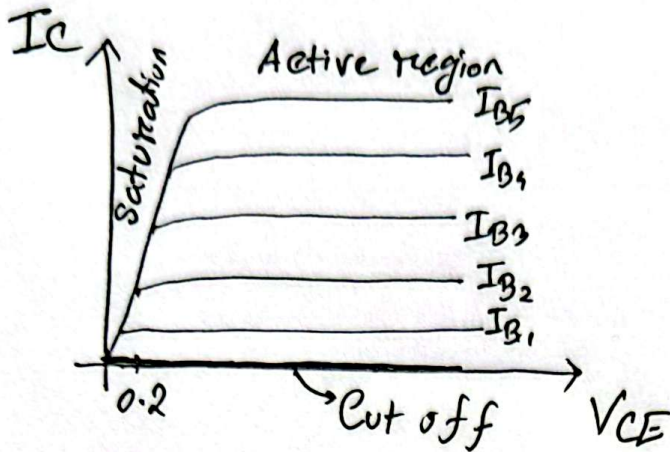



Q-1) BJT

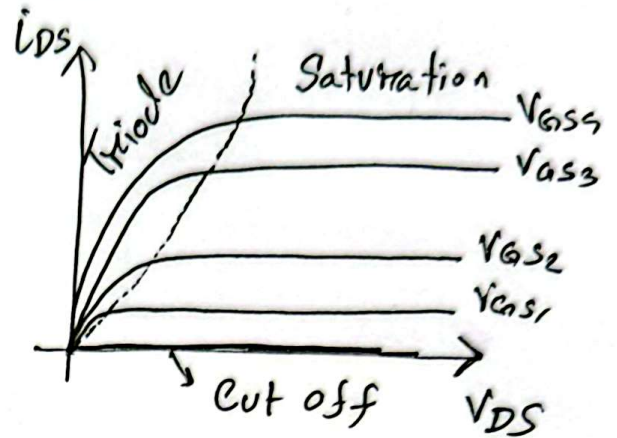



MOSFET




b)

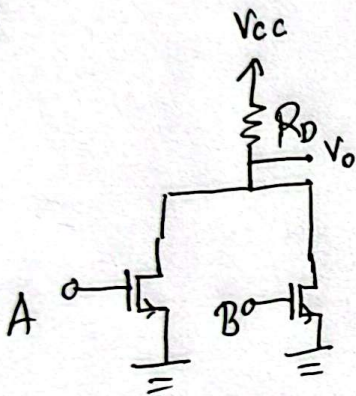


$$V_A = 0$$

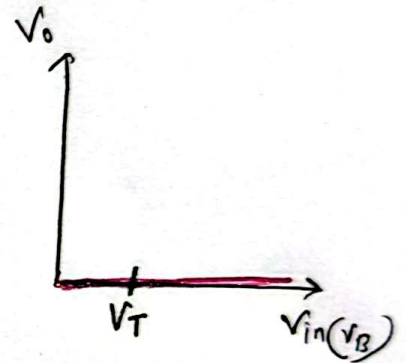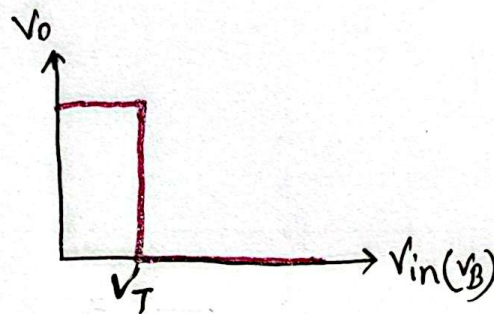


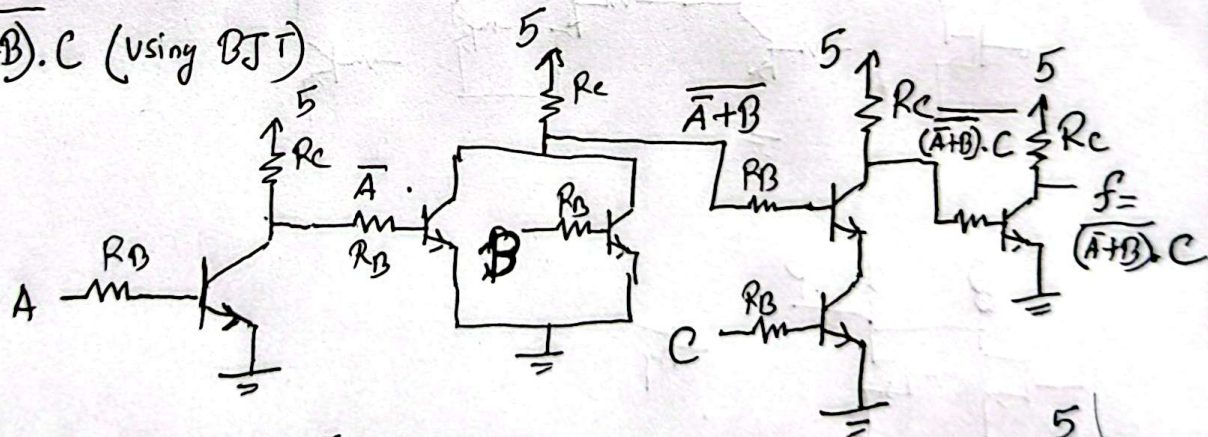
Q2 a) $f = (\overline{A+B}) \cdot C$ (using BJT)



b) $f = (\overline{A+B}) + A + CD$

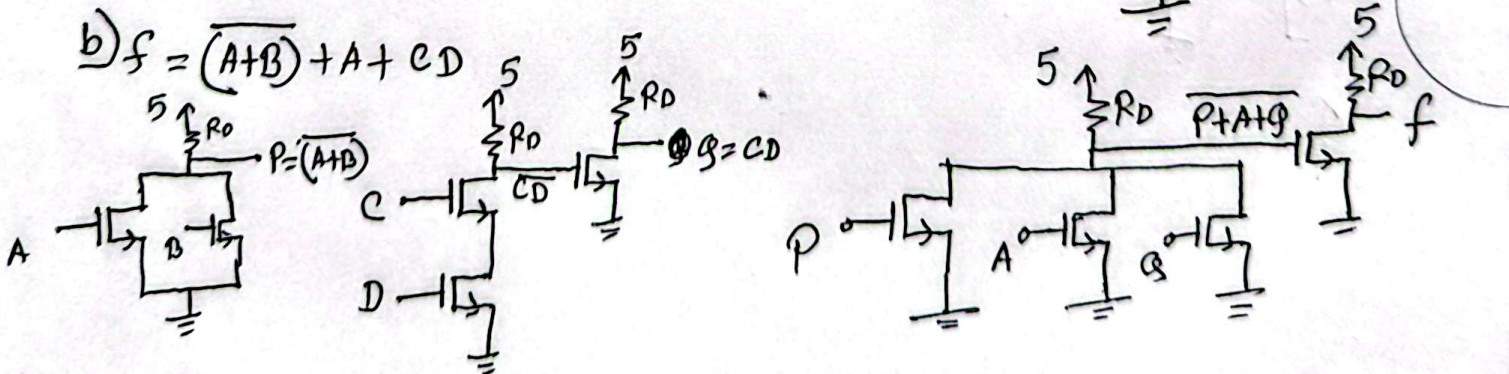

Q3

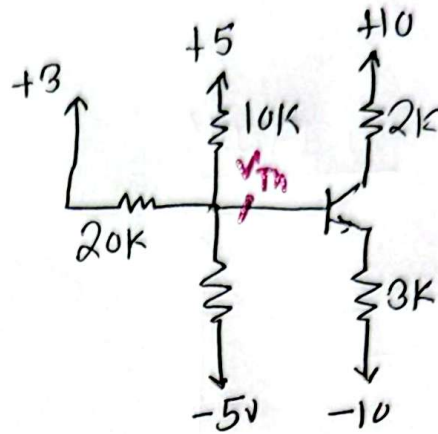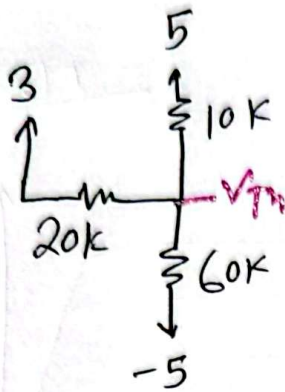


Theremin's Theorem

KCL


$$\frac{V_{Th}-5}{10} + \frac{V_{Th}+5}{60} + \frac{V_{Th}-3}{20} = 0$$

$$V_{Th} = 3.4$$

R_{Th}

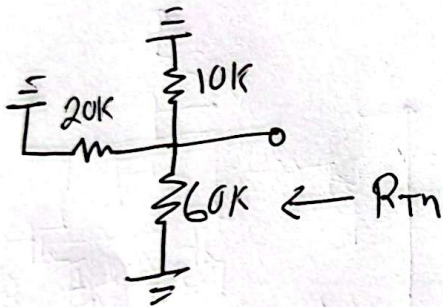
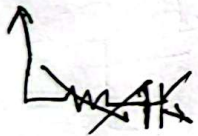
$$R_{Th} = 20 \parallel 60 \parallel 10 = 6k$$



Assuming Saturation Mode

KVL $3.4 = 6i_B + 0.8 + 3i_E - 10$

$$\Rightarrow 6i_B + 3i_E = 12.6 \quad \text{--- (i)}$$

KVL $10 = 2i_C + 0.2 + 3i_E - 10$

$$\Rightarrow 2i_C + 3i_E = 19.8 \quad \text{--- (ii)}$$

KCL $i_E = i_C + i_B$

$$\Rightarrow i_B + i_C - i_E = 0 \quad \text{--- (iii)}$$

$$i_B = 0.1 \text{ mA}$$

$$i_C = 3.9 \text{ mA}$$

$$i_E = 4 \text{ mA}$$

$$\frac{i_C}{i_B} = \frac{3.9}{0.1} = 39 < 100$$

Correct Assumption

Saturation

Q3

Given,

$$V_G = 4V$$

$$V_T = 1V$$

$$I_{DS} = 2mA$$

$$K = 4mA/V^2$$

Assuming the MOSFET is in Saturation region

$$I_{DS} = \frac{1}{2} K [V_{GS} - V_T]^2$$

$$\Rightarrow 2 = \frac{1}{2} \times 4 [4 - V_S - 1]^2$$

$$\Rightarrow 1 = (3 - V_S)^2$$

$$\Rightarrow 9 - 6V_S + V_S^2 = 1$$

$$\Rightarrow V_S^2 - 6V_S + 8 = 0$$

$$\Rightarrow V_S = 4 \text{ or } 2V$$

$$\text{if } V_S = 4 \quad V_{GS} = 0 < V_T \quad \times$$

$$\text{if } V_S = 2 \quad V_{GS} = 2V > V_T \quad \checkmark$$

$$\therefore V_S = 2$$

$$2 = \frac{10 - V_D}{1} \quad \therefore V_D = 8V$$

$$V_{DS} = 8 - 2 = 6V$$

$$V_{ov} = V_{GS} - V_T = 2 - 1 = 1$$

$$\therefore V_{GS} > V_T$$

$$V_{DS} \geq V_{ov}$$

Assumption is correct


$$\therefore \boxed{V_D = 8V}$$

95

M_2 - Saturation

$$V_{G_1} = V_{D_1}$$
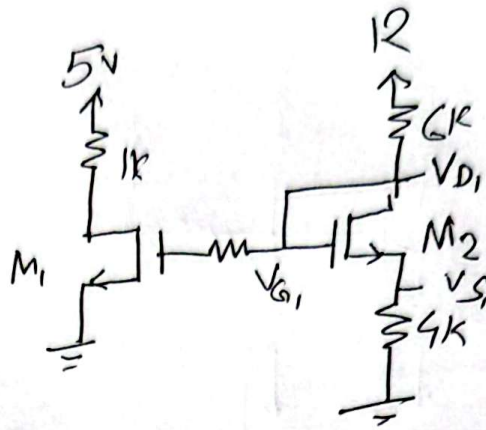
$$\begin{aligned} I_{D_1} &= \frac{K_n}{2} [V_{G_{S_1}} - V_T]^2 \\ &= \frac{2}{2} [V_{G_7} - V_{S_1} - V_T]^2 \\ &= [V_{D_1} - V_{S_1} - V_T]^2 \end{aligned}$$



$$\Rightarrow V_{D1} = 12 - \frac{3}{2} V_{S1} \quad \text{--- (i)}$$

$$\Rightarrow \frac{V_{S_1}}{4} = \left[12 - \frac{3V_{S_1}}{2} - 1 \right]^2 = \left[12 - \frac{3}{2}V_{S_1} - V_{S_1} - 1 \right]^2$$

$$\Rightarrow \frac{V_{S1}}{4} = \left[11 - \frac{5}{2} V_{S1} \right]^2$$

$$\Rightarrow \frac{V_{S1}}{4} = 121 - 55 V_{S1} + \frac{25}{4} V_{S1}^2$$

$$\Rightarrow \frac{25}{4} V_{S_1}^2 - \frac{221}{4} V_{S_1} + 121 = 0$$

$$\Rightarrow 25V_{S_1}^2 - 221V_{S_1} + 484 = 0$$

$$V_{S1} = 4 \text{ or } 4.84$$

if $V_{S1} = 4V$

$$v_{p1} = 6$$

$$\therefore V_{G1} = 6$$

$$V_{GS1} = 2V > V_T$$

$$\therefore V_{S_1} = 4$$

$$\therefore I_{R_{D1}} = \frac{12-6}{6} = 1 \text{ mA}$$

if $V_{S1} = \cancel{4V} 4.84V$

$$V_{D_1} = 4.79$$


$$V_{G1} = 4.79$$

$$V_{GS_1} < V_T \quad \times$$

Assuming Triode Mode

$$V_{S2} = 0$$

$$V_{G2} = 6V$$

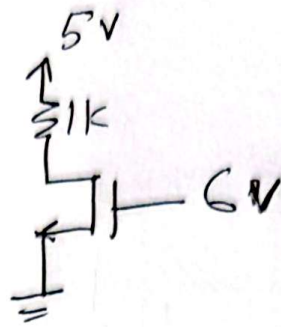

$$I_D = k \left[V_{GS2} - V_T - \frac{1}{2} V_{DS2} \right] V_{DS2}$$

$$\Rightarrow \frac{5 - V_{D2}}{1} = \frac{1}{2} \left[V_{G2} - V_T - \frac{1}{2} V_{D2} \right] V_{D2}$$

$$\Rightarrow 5 - V_{D2} = \frac{1}{2} \left[6 - 1 - \frac{1}{2} V_{D2} \right] V_{D2}$$

$$\Rightarrow 10 - 2V_{D2} = 5V_{D2} - \frac{1}{2} V_{D2}^2$$

$$\Rightarrow V_{D2}^2 - 14V_{D2} + 20 = 0$$

$$\Rightarrow V_{D2} = 12.385, 1.615V \checkmark$$

$$V_{DS} > V_{OV} \quad \checkmark \quad \times$$

$$\begin{aligned} V_{DS} &\rightarrow V_{OV} \\ V_{DS} &< V_{OV} \end{aligned}$$

$$\begin{aligned} I_{RD2} &= \frac{5 - 1.615}{1} \\ &= 3.385 \text{ mA} \end{aligned}$$

$$V_O = V_{D2} = 1.615V$$

$$I_{RD1} = 1 \text{ mA}$$

$$I_{RD2} = 3.385 \text{ mA}$$