


Assignment - 3 [Solution]

1 #

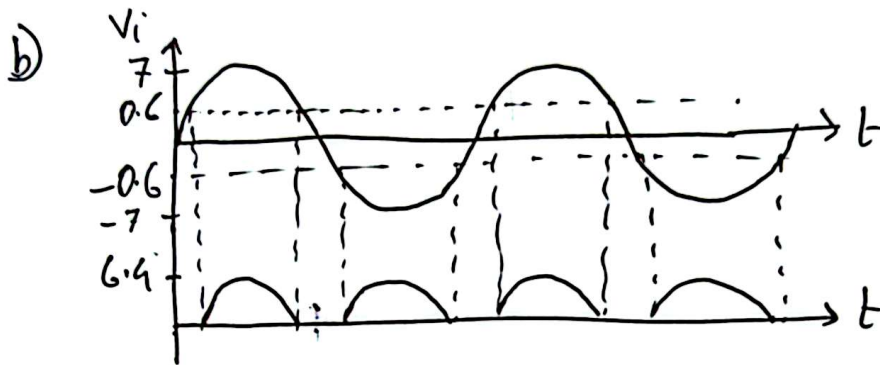a) $V_s(t) = 7 \sin(400\pi t)$

$\therefore f_i = 200 \text{ Hz}$

$f_o = 2 \times f_i \quad [\text{Full wave Rectifier}]$
 $= 400 \text{ Hz}$




c) $V_{DC} = \frac{2V_m}{\pi} - 2V_{D0} \quad ; \quad V_m = 7 \text{ V}$
 $= 3.86 \text{ V} \quad V_{D0} = 0.3$

d) $C = 100 \mu\text{F}$ $f_r = 2 \times 200 \text{ Hz} = 400 \text{ Hz}$
 $R = 5 \text{ K}$ $V_{D0} = 0.3$
 $V_p = V_m - 2V_{D0} = 6.4 \text{ V}$
 $\therefore V_{\pi(p-p)} = \frac{V_p}{f_r R C}$
 $= \frac{6.4}{400 \times 5 \times 10^3 \times 100 \times 10^{-6}} = 0.032 \text{ V}$

e) $V_{DC} = V_p - \frac{V_{\pi(p-p)}}{2} = 6.4 - \frac{0.032}{2} = 6.384 \text{ V}$

2#

a)

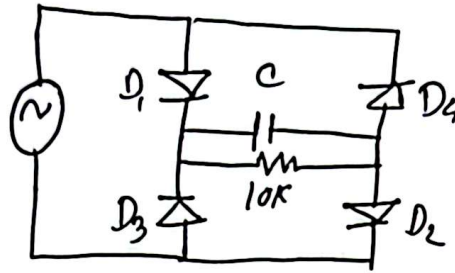

b)

$$V_m = 10, V_{D0} = 0.8$$

$$V_p = V_m - 2V_{D0} = 8.4$$

$$V_{\pi(p-p)} = 31 \times V_p = 8.4 \times \frac{3}{100} = 0.252$$

c)

$$V_{DC} = V_{Avg} = V_p - \frac{V_{\pi(p-p)}}{2} = 8.4 - \frac{0.252}{2} = 8.274$$

d)

$$V_{\pi(p-p)} = \frac{V_p}{f_{\pi} R C}$$

$$\Rightarrow C = \frac{8.4}{100 \times 10 \times 10^3 \times 0.252}$$

$$= 33.33 \times 10^{-6} = 33.33 \mu F$$

$f_i = 100 \text{ Hz}$
 $f_{\pi} = 100 \text{ Hz}$
 $R = 10 \times 10^3$

3

b) $C = 8 \mu F$ $R = 10 K$

$$F_R = 100 Hz \quad \therefore F_i = \frac{F_R}{2} = 50 Hz$$

$$V_{00} = 1 V$$

$$I_{Avg} = 0.75 mA \quad \therefore V_{Avg} = 0.75 \times 10 = 7.5 V$$

$$V_{Avg} = V_p - \frac{V_{\pi(p-p)}}{2}$$

$$= V_p - \frac{V_p}{2 f_n R C} = V_p \left(1 - \frac{1}{2 f_n R C} \right)$$


$$\therefore V_p = \frac{V_{Avg}}{\left(1 - \frac{1}{2 f_n R C} \right)}$$

$$= 8 V$$

$$\therefore V_m = V_p + 2 V_{00} = 10 V$$

$$\therefore V_{in} = 10 \sin(2\pi 50 t)$$

$$= 10 \sin(100\pi t)$$

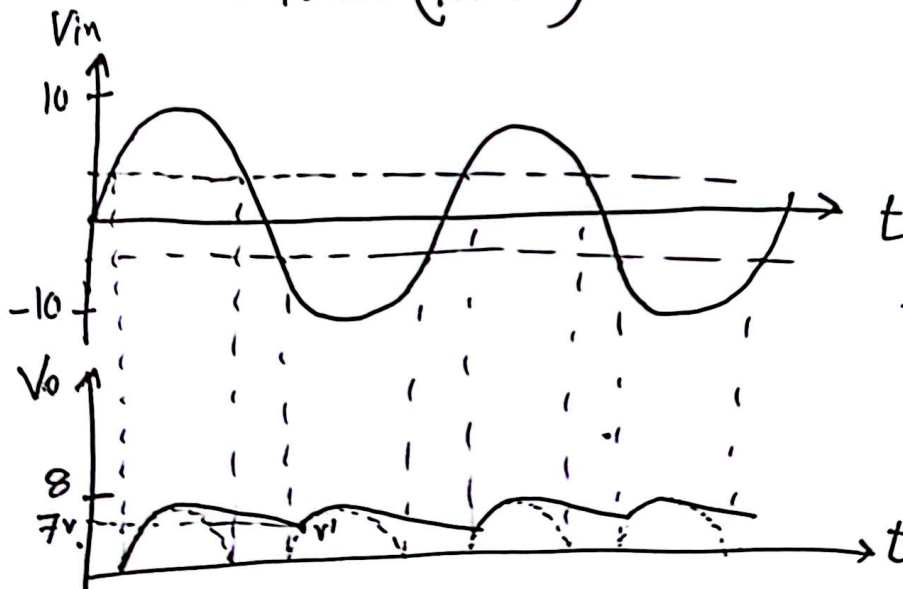



$$V_{\pi(p-p)} = \frac{8}{100 \times 8 \times 10^{-6} \times 10 \times 10^3}$$

$$= 1 V$$


$$V_{\pi(p-p)} = V_p - V'$$

$$\Rightarrow V' = 8 - 1 = 7 V$$



4#

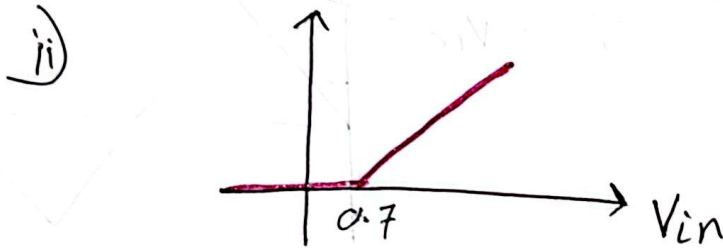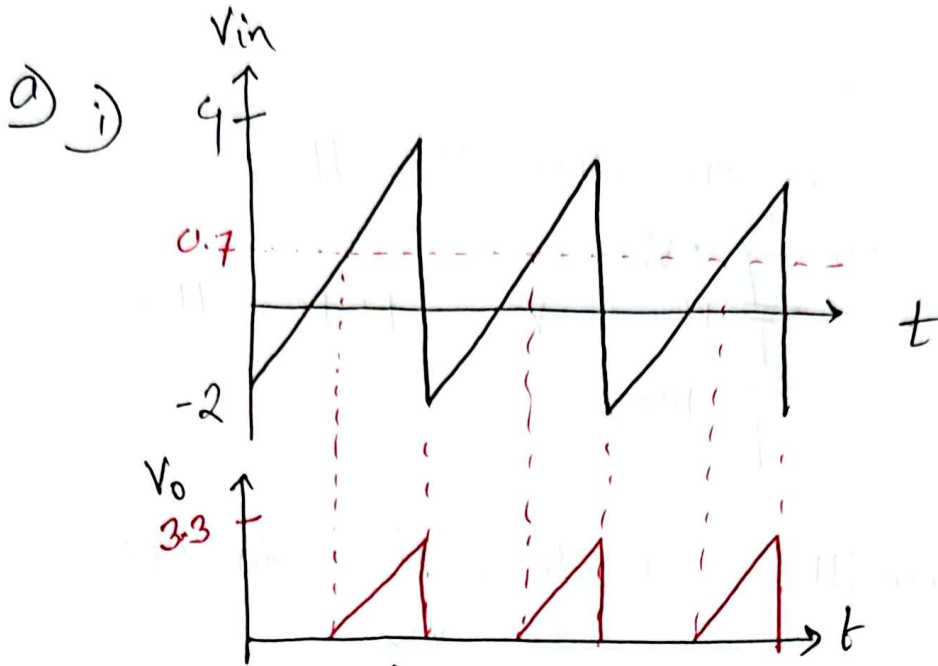

b) for, $V_{in} = 20V$

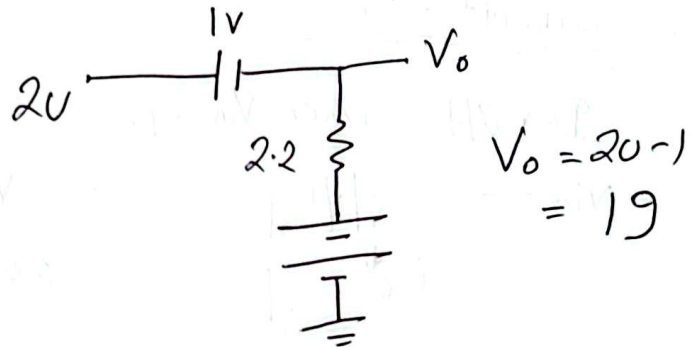


for, $V_{in} = -5V$

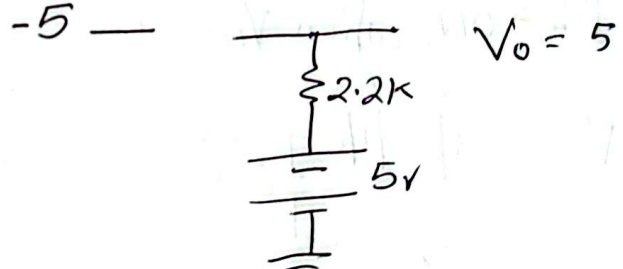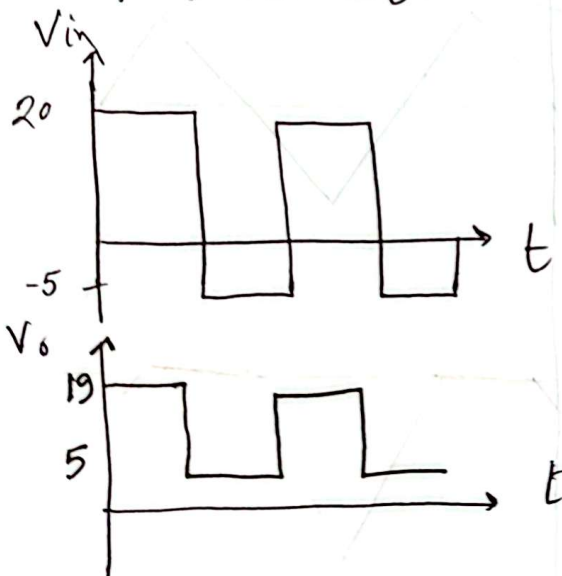

5#

Circuit - 2


Diode will be on when $V_{in} > 11V$

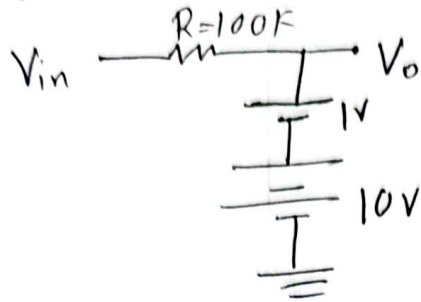


$$V_o = 1 + 10 = 11V$$

if $V_{in} < 11V$

Diode will remain off [R.B]

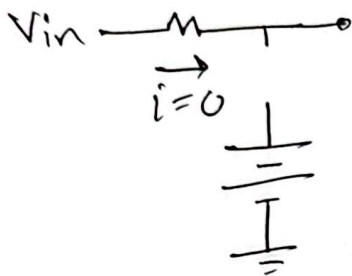


$$V_o = V_{in}$$

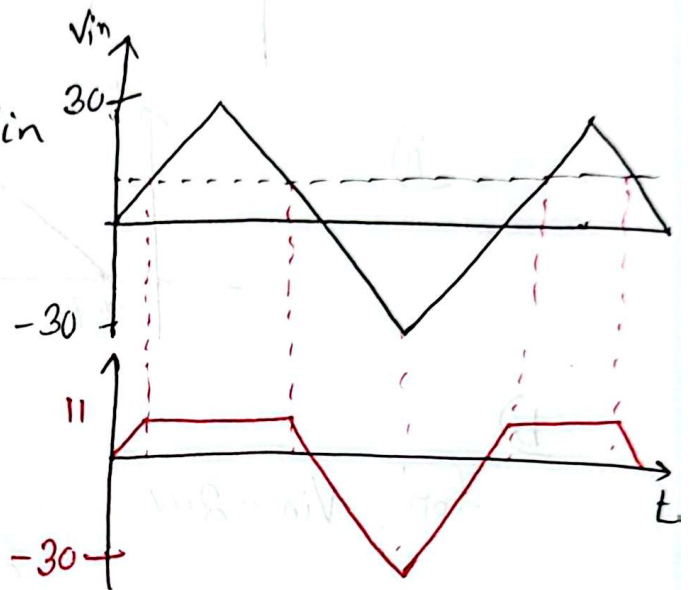

Circuit - 3

D → off, when $V_{in} > 4V$

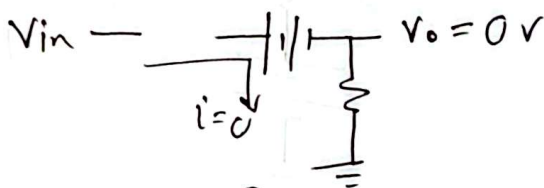

D → ON, when $V_{in} < 4V$

