

BRAC UNIVERSITY
Department of Computer Science and Engineering

Quiz 04
Semester: Summer 2025


Time: 15 min
Full Marks: 14

Name:	ID:	Section:
-------	-----	----------

CSE 251: Electronic Devices and Circuits

1. [CO1] 4
Show the I-V characteristics graph of BJT (I_c vs V_{CE}). Identify the operating regions in the graph.

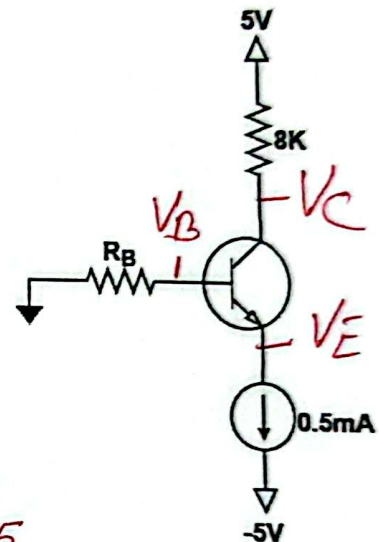2. [CO2] 10
For the transistor in the following circuit, $\beta = 75$, $V_{BE, active} = V_{BE, sat} = 0.7$ V.
Determine the value of R_B that results in transistor operating in active mode with $V_{CE} = 2$ V



2) $I_E = 0.5 \text{ mA}$

$$I_E = (1 + \beta) I_B$$

$$\therefore I_B = \frac{0.5}{1 + 75} = 0.0066 \text{ mA}$$

$$I_c = \beta I_B = 75 \times 0.0066 = 0.495$$

$$I_c = \frac{5 - V_c}{8}$$

$$\therefore V_c = 5 - 8I_c = 5 - (8 \times 0.495) = 1.04 \text{ V}$$

$$V_{CE} = 2 \text{ V}$$

$$\Rightarrow V_c - V_E = 2 \text{ V}$$

$$\therefore V_E = -0.96$$

$$V_{BE} = 0.7$$

$$\Rightarrow V_B - V_E = 0.7$$

$$\therefore V_B = -0.26$$

$$I_B = \frac{0 - V_B}{R_B}$$
$$\Rightarrow R_B = \frac{0 + 0.26}{0.0066} = 39.39 \text{ K}$$