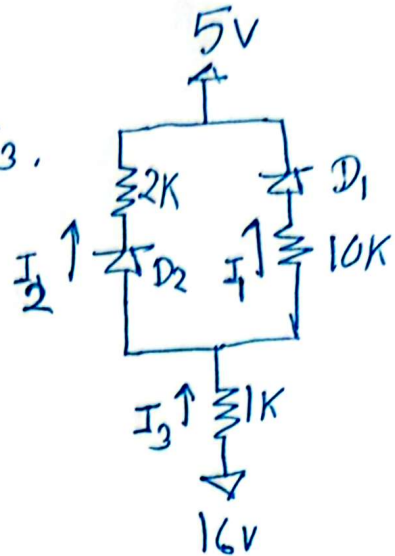


Example - 1


Calculate the values of I_1, I_2, I_3 .

Where $V_{DO} = 0.8V$.

[Validate your assumption]



Assume both D_1 & $D_2 \rightarrow ON$

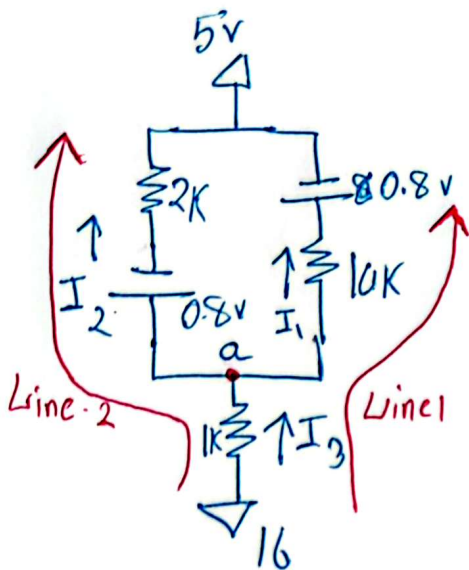

Line-1

$$16 = I_3 + 10I_1 + 0.8 + 5$$

$$10I_1 + I_3 = 10.2 \quad \text{--- (i)}$$

Line-2

$$16 = I_3 + 0.8 + 2I_2 + 5$$

$$\Rightarrow 2I_2 + I_3 = 10.2 \quad \text{--- (ii)}$$

KCL at node a

$$I_3 = I_1 + I_2$$

$$\Rightarrow I_1 + I_2 - I_3 = 0 \quad \text{--- (iii)}$$

Solving eqⁿ (i), (ii) & (iii)

$$I_1 = 0.6375 \text{ mA}$$

$$I_2 = 3.1875 \text{ mA}$$

$$I_3 = 3.825 \text{ mA}$$

$$I_2 > 0, I_1 > 0$$


$$I_3 > 0$$

Assumption is correct

Example -2

Calculate I_{D1} and I_{D2} using method of assumed states.

$$V_{D0} = 0.7V$$

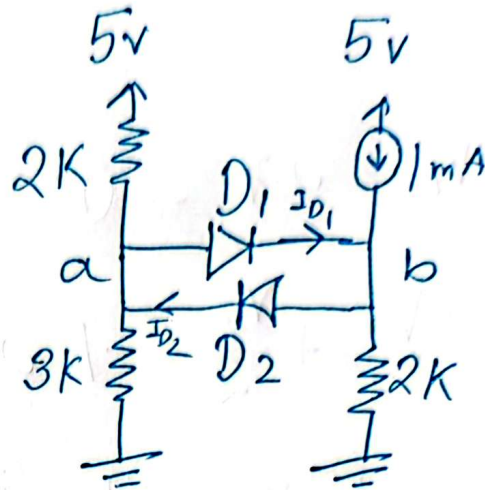


Assume :
 $D_1 \rightarrow$ reverse bias
 $D_2 \rightarrow$ Forward bias

$$V_b - V_a = 0.7 \quad \text{--- (i)}$$

$$\frac{V_b}{2} + \frac{V_a - 5}{2} + \frac{V_a}{3} - 1 = 0$$

$$\Rightarrow 5V_a + 3V_b = 21$$

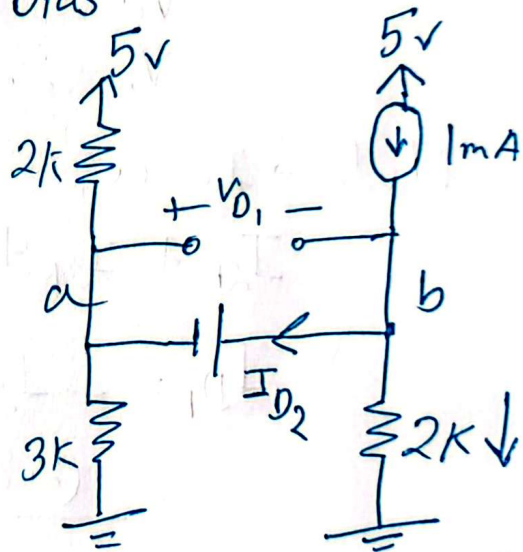

\rightarrow (ii)

Solving eqn (i) & (ii)

$$V_a = 2.3625$$

$$V_b = 3.0625$$

KCL at b

$$1 - I_{D2} = \frac{V_b}{2}$$

$$\therefore I_{D2} =$$

$$1 = I_{D2} + \frac{V_b}{2}$$

$$\Rightarrow I_{D2} = 1 - \frac{3.0625}{2}$$

$$= -0.53125 < 0$$

Wrong Assumption


Assume

$D_1 \rightarrow$ Forward bias $D_2 \rightarrow$ Reverse bias

$$V_a - V_b = 0.7 \quad \text{--- (i)}$$

$$\frac{V_a - 5}{2} + \frac{V_a}{3} + \frac{V_b}{2} - 1 = 0$$
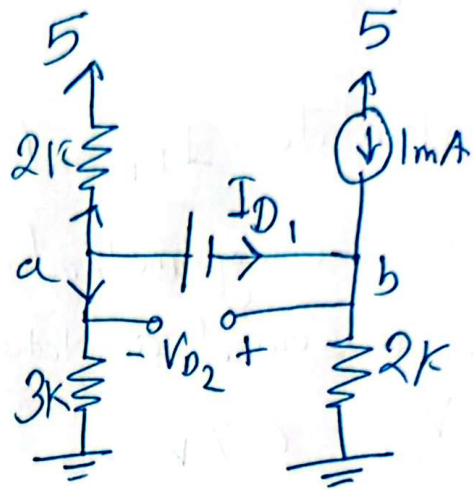
$$\Rightarrow 5V_a + 3V_b = 21 \quad \text{--- (ii)}$$



Solving eqn (i) & (ii)

$$V_a = 2.8875$$

$$V_b = 2.1875$$

Node \rightarrow ~~Da~~ a

$$I_{2k} + I_{3k} + I_{D1} = 0$$

$$\Rightarrow I_{D1} = -I_{2k} - I_{3k}$$

$$= -\frac{(2.8875 - 5)}{2} - \frac{(2.8875)}{3}$$

$$= 0.09375 > 0$$

$$V_{D2} = V_b - V_a$$

$$= 2.1875 - 2.8875$$

$$= -0.7 < 0.7 \text{ V}$$

$$\boxed{\begin{matrix} I_{D1} > 0 \\ V_{D2} < 0.7 \end{matrix}}$$

$$I_{D1} = 0.09375 \text{ mA}$$

$$I_{D2} = 0$$

Assumption is correct


Example-3

Find the voltage V
and I_{D1} & I_{D2} ..

$$V_{D0} = 0.7V$$

Assume:

Both $D_1, D_2 \rightarrow ON$

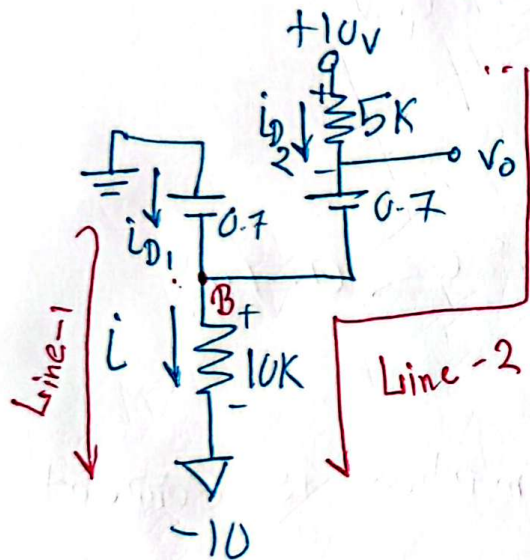

Line-1

$$0 = 0.7 + 10i - 10$$

$$\Rightarrow i = 0.93 \text{ mA}$$

Line-2

$$10 = 5i_{D2} + 0.7 + 10i - 10$$

$$\Rightarrow 5i_{D2} + 10 \times (0.93) = 19.3$$


$$\Rightarrow i_{D2} = 2 \text{ mA} \quad [\because i = 0.93 \text{ mA}]$$

KCL at Node B

$$i_{D1} + i_{D2} = i$$

$$\Rightarrow i_{D1} = 0.93 - 2 \text{ mA} = -1.07 < 0$$

Invalid Assumption

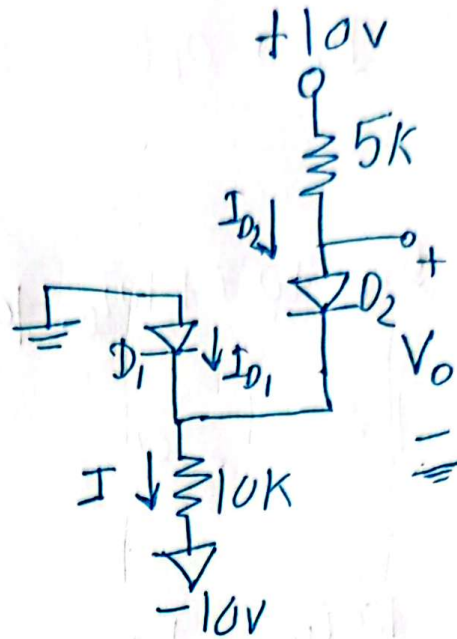

Assume: $D_1 \rightarrow \text{off}$ $D_2 \rightarrow \text{ON}$

Line-1

$$10 = 5i_{D2} + 0.7 + 10i_{D2} - 10$$

$$i_{D2} = 1.286 > 0$$

$$V_e = 10i_{D2} - 10$$

$$= 10 \times 1.286 - 10 = 2.86 \text{ V}$$

$$V_{D1} = V_A - V_e$$

$$= 0 - 2.86 = -2.86 < 0.7 \text{ V}$$

$$I_{D2} > 0$$

$$V_{D1} < 0.7$$


Assumption is correct

$$i_{D1} = 0$$


$$i_{D2} = 1.286 \text{ mA}$$

$$V_o = 0.7 + 10i_{D2} - 10$$


$$= 3.56 \text{ V}$$

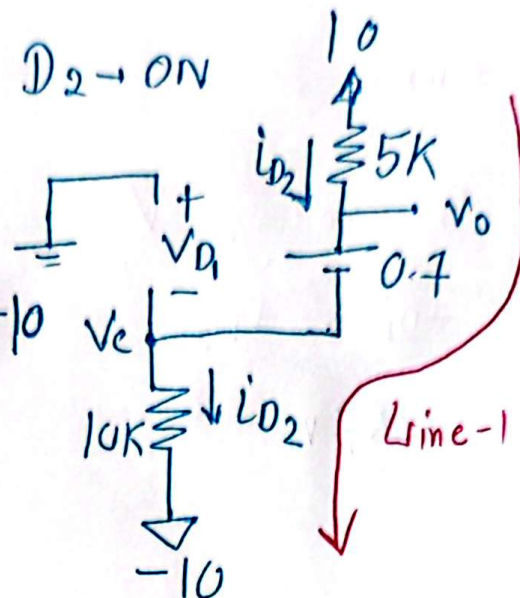

②

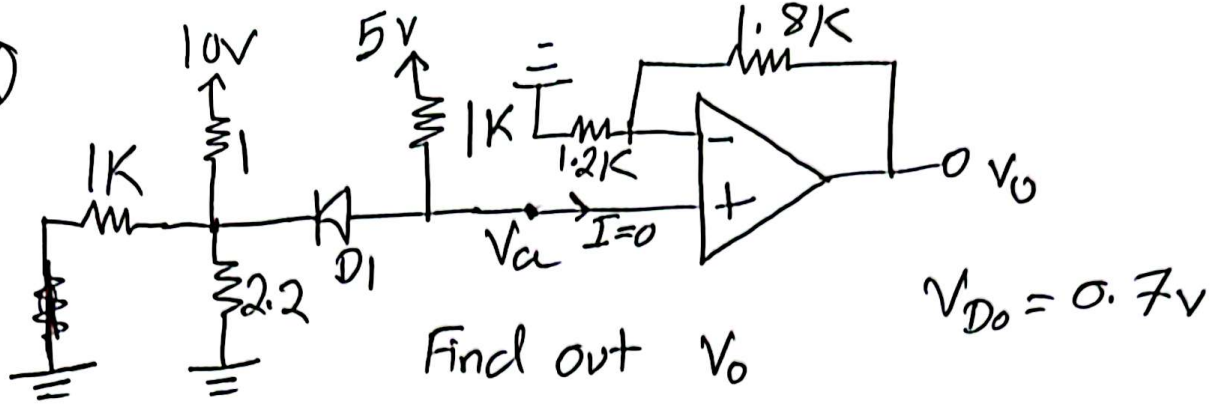

Assume $D_1 \rightarrow$ off

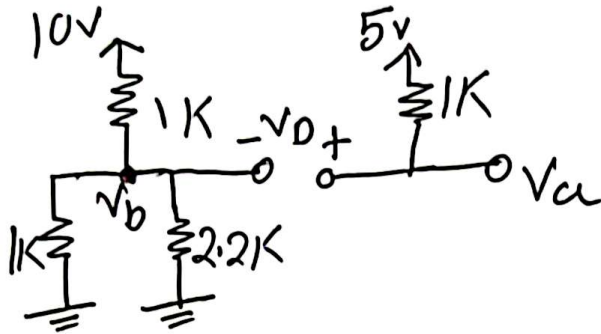

$$V_a = 5V$$


$$V_b = \frac{(1 \parallel 2.2)}{(1 \parallel 2.2) + 1} \times 10$$

$$= 4.07V$$

$$V_D = V_a - V_b = 5 - 4.07 = 0.93V > 0.7V$$

Assumption is incorrect.

$D_1 \rightarrow$ on

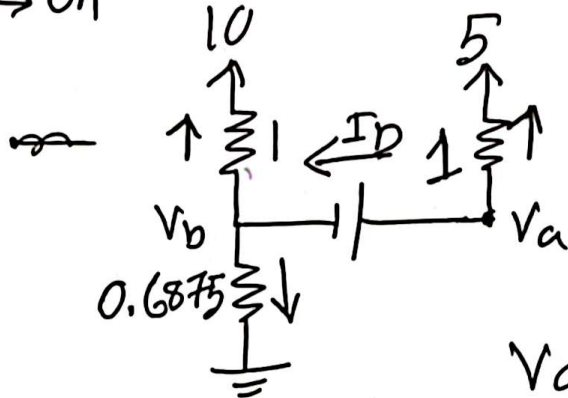

Super Node

$$\frac{V_a - 5}{1} + \frac{V_b - 10}{1} + \frac{V_b - 0}{0.6875} = 0$$

①

$$V_a - V_b = 0.7V$$



$$V_a = 4.84$$

$$I_D = \frac{5 - V_a}{1} = 0.16 \text{ mA} > 0 \rightarrow \text{Correct Assumption}$$

$$\therefore V_o = \left(1 + \frac{1.8}{1.2}\right) \times 4.84$$

$$= 12.1V$$

③

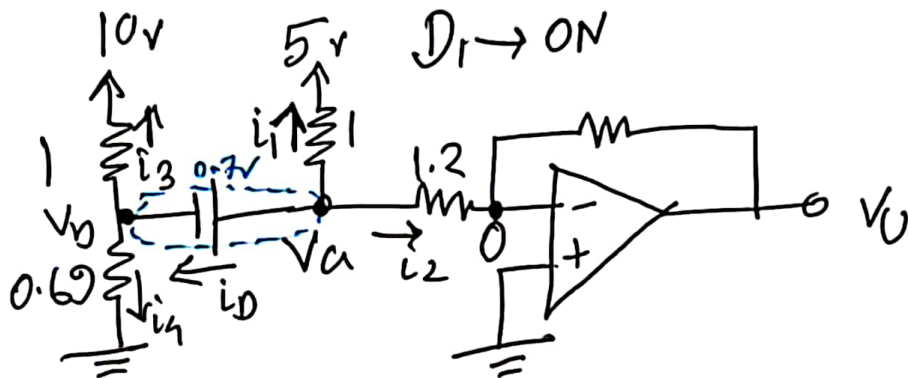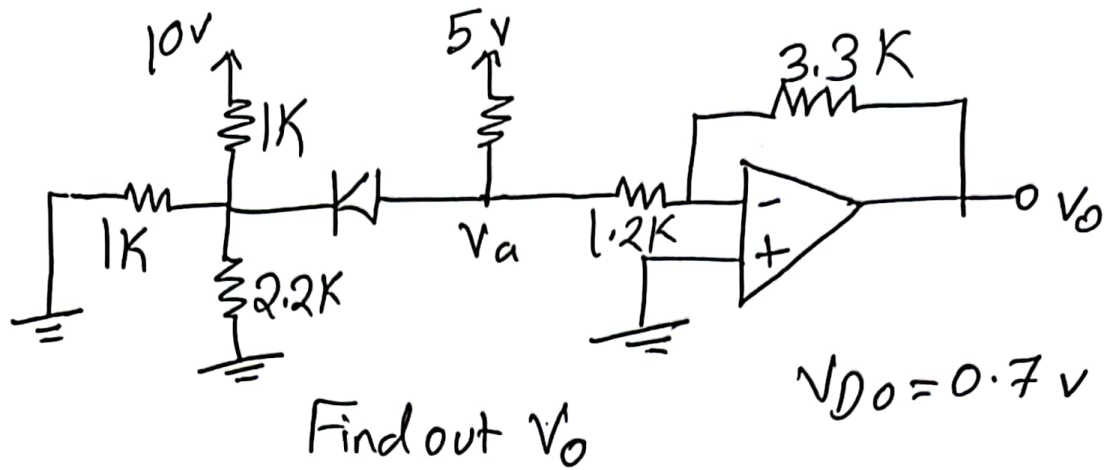

$$\frac{V_a - 5}{1} + \frac{V_a - 0}{1.2} + \frac{V_b - 10}{1} + \frac{V_a - 0}{0.69} = 0 \quad \text{--- (i)}$$

$$V_a - V_b = 0.7\text{V} \quad \text{--- (ii)}$$

$$V_a = 3.9\text{V}$$

$$V_b = 3.2\text{V}$$

KCL at Node V_a

$$i_1 + i_2 + i_0 = 0$$



$$\Rightarrow \frac{3.9 - 5}{1} + \frac{3.9 - 0}{1.2} + I_0 = 0$$

$$\Rightarrow -1.1 + 3.25 + I_0 = 0$$

$$\therefore I_0 = -2.15\text{mA} < 0\text{mA}$$

So Assumption is incorrect

So D_1 is dB

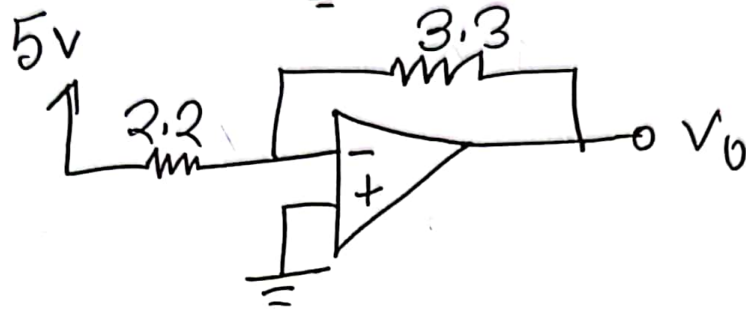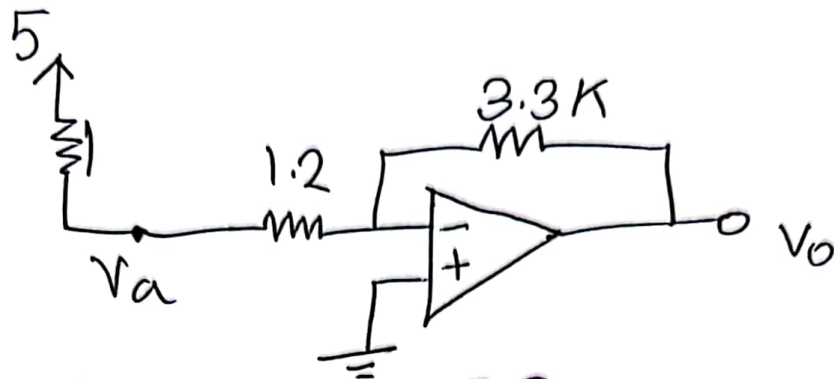

$$\begin{aligned} V_o &= -\frac{R_f}{R_i} \times V_{in} \\ &= -\frac{3.3}{2.2} \times 5 \\ &= -\cancel{6.75} \\ &= -7.5V \end{aligned}$$