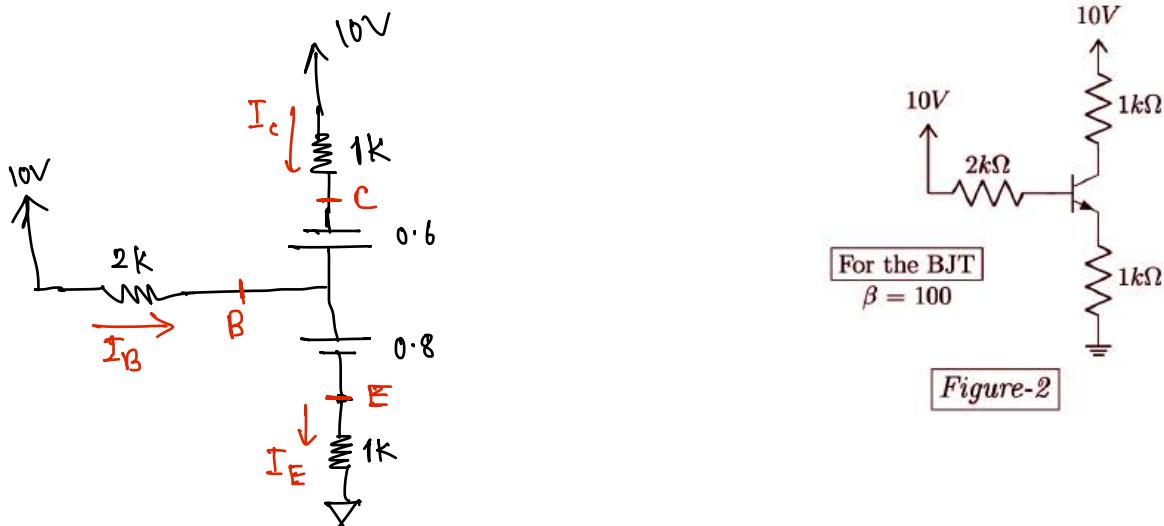


SPRING 2025

Analyze the circuit in Figure-2, and calculate I_B , I_C , I_E , V_C & V_E using the method of assumed states. You must validate your assumption.



Assume Saturation mode. Based on the equivalent circuit.

Applying KVL across Base to Emitter line,

$$-10 + 2I_B + 0.8 + I_E + 0 = 0$$

or,
$$\boxed{2I_B + I_E = 9.8} \quad \text{--- (1)}$$

Applying KVL across Collector to Emitter Line,

$$-10 + I_C - 0.6 + 0.8 + I_E + 0 = 0$$

or,
$$\boxed{I_C + I_E = 9.8} \quad \text{--- (2)}$$

And we know for all condition,
$$\boxed{I_C + I_B = I_E} \quad \text{--- (3)}$$

Solving eq (1) (2) (3),

$$\left| \begin{array}{l} I_C = 3.92 \text{ mA} \\ I_B = 1.96 \text{ mA} \\ I_E = 5.88 \text{ mA} \end{array} \right| \quad \left| \begin{array}{l} V_C = 10 - I_C \times 1\text{k} \\ = 6.08 \text{ V} \\ V_E = I_E \times 1\text{k} \\ = 5.88 \text{ V} \end{array} \right|$$

Verify:



$$\frac{I_C}{I_B} = \frac{3.92}{1.96} = 2 < \beta = 100$$

verified.

Design a circuit with boolean inputs A, B, and C using BJTs to implement the boolean logic Function.

$$f = \overline{A} \cdot B + \overline{B} \cdot C + \overline{C} \cdot A$$

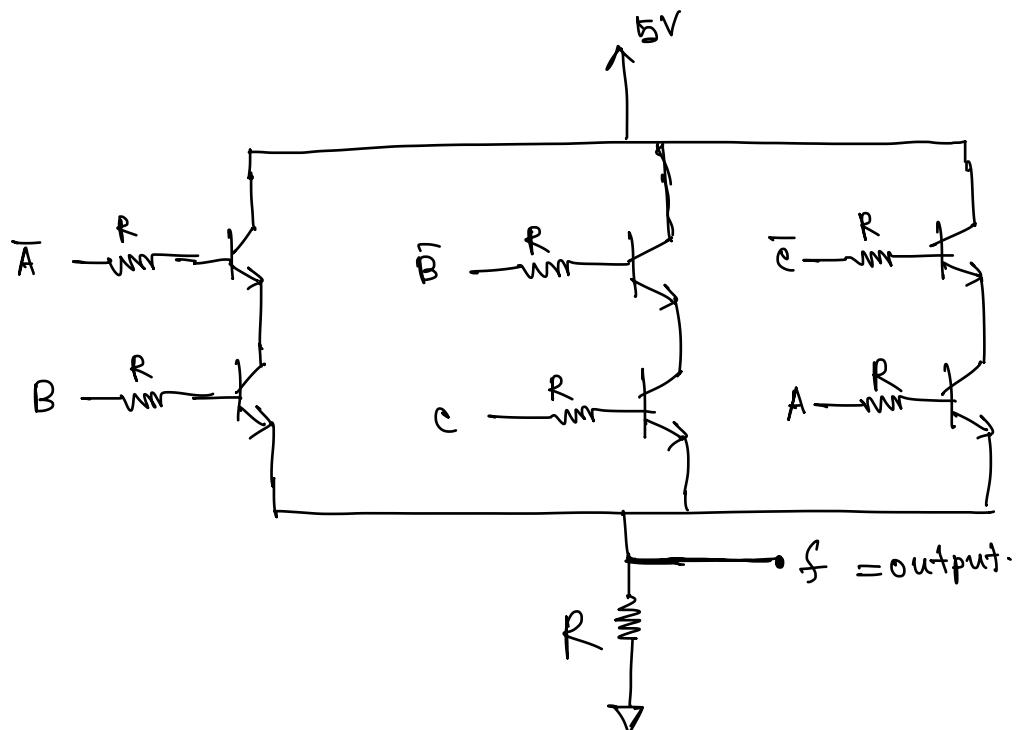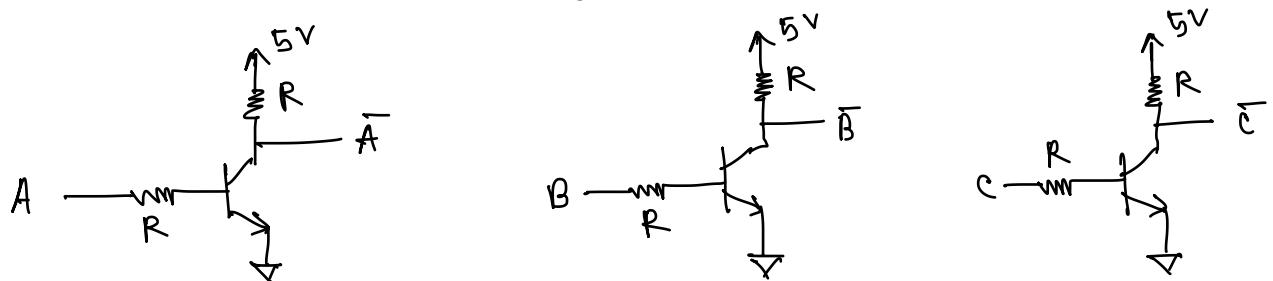BJT means a resistor at every input terminal.



* You need to draw separate NOT Gates for each boolean input. Here, three separate for each of A, B, C.

Analyze the circuit in Figure-2, and calculate I_B , I_C , I_E , V_C & V_E using the method of assumed states. You must validate your assumption.


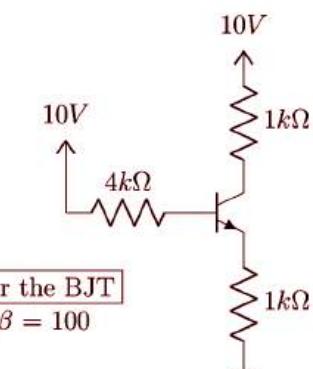


Figure-2

FALL 2024

Analyze the circuit in Figure-1 and calculate the values of I_B , I_C , I_E , and V_O using the method of assuming states. You must validate your assumption. Here, $\beta = 100$.

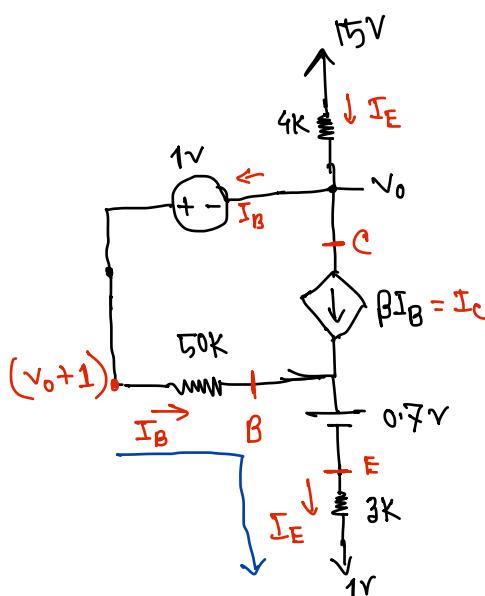Based on the annotations in the given circuit diagram (blue), it is clear that I_E goes through $4k\Omega$ and $3k\Omega$. Let's assume Active Mode.



KCL at V_o ensures,

$$I_E = I_B + I_C.$$

$$\text{So, } I_E = \frac{15 - V_o}{4} \quad \text{--- (1)}$$

Applying KVL from $(V_o + 1)$ node to emitter line.

$$-(V_o + 1) + 50I_B + 0.7 + 3I_E + 1 = 0 \quad \text{--- (2)}$$

In active mode, $I_E = (\beta + 1) I_B$ or, $I_E = 101 I_B$

from equation (1), $101 I_B = \frac{15 - V_o}{4}$ or, $V_o = 15 - 404 I_B$

from equation (2), $50I_B + 3(101I_B) + 1.7 = V_o + 1 = 15 - 404I_B + 1$

or, $50I_B + 303I_B + 404I_B = 16 - 1.7 = 14.3$

or, $I_B = 0.018 \text{ mA}$

So, $I_E = 101 I_B = 1.907 \text{ mA}$

$I_C = \beta I_B = 1.8 \text{ mA}$

$V_B = 7.728 \text{ V}$

* verified $V_c = V_o = 7.728 \text{ V}$

$$\begin{aligned} V_E &= 3I_E + 1 \\ &= 6.721 \text{ V} \end{aligned}$$

So, $V_{CE} = \boxed{1 \text{ V} > 0.2 \text{ V}}$

verified.

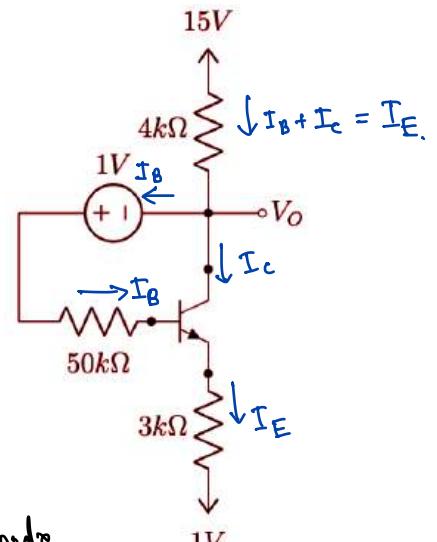


Figure-1

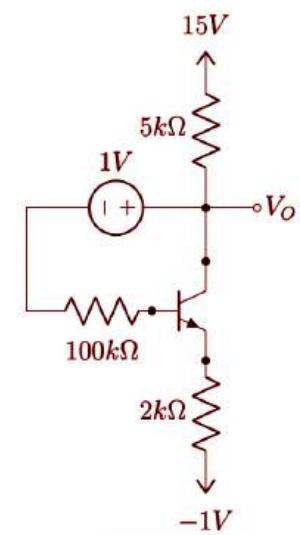




Figure-1

SUMMER 2024

Karim designed a BJT circuit. When his friend Rahim saw it, he claimed that the BJT would operate in Active mode. Then Rahim built a circuit and asked Karim to figure out the operating mode of the BJT.

Calculate I_B , I_C , I_E , V_{CE} in Karim's circuit and determine whether Rahim was correct or not.

Let's assume Active mode,

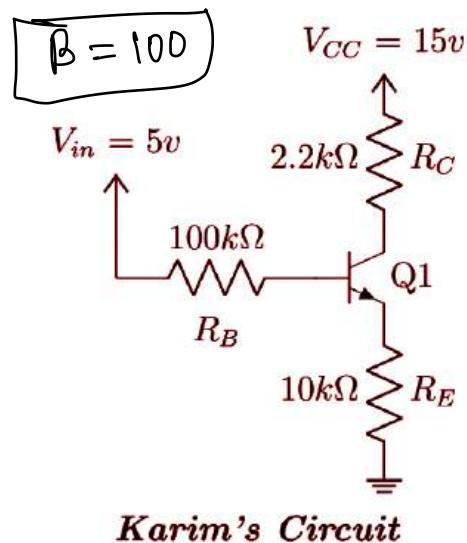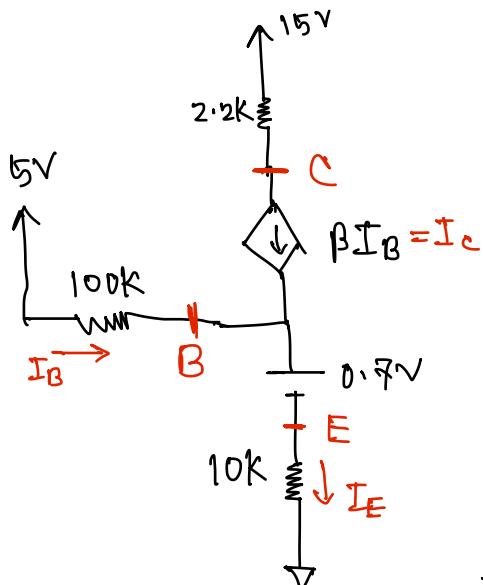

Apply KVL from Base line to Emitter line,

$$-5 + 100I_B + 0.7 + 10I_E + 0 = 0$$

But in Active mode, $I_E = (\beta + 1) I_B = (100 + 1) I_B = 101 I_B$

$$\text{So, } 100I_B + 10(101I_B) = 5 - 0.7 = 4.3$$

$$\text{or, } I_B = 0.0038 \text{ mA.}$$

$$\text{So, } I_C = \beta I_B = 100I_B = 0.38 \text{ mA}$$

$$\text{and } I_E = 101I_B = 0.391 \text{ mA}$$

$$\text{So, } V_C = 15 - 2.2I_C = 14.148 \text{ V}$$

$$V_E = 10I_E = 3.91 \text{ V} \quad \text{* Verified:}$$

$$\begin{aligned} \text{So, } V_{CE} &= 14.148 - 3.91 \\ &= 10.238 \text{ V} \end{aligned}$$



$$V_{CE} = 10.23 \text{ V} > 0.2 \text{ V}$$

verified

Active mode. Rahim was correct.

Analyze Rahim's circuit and Calculate I_B , I_C , I_E , V_{CE} to help Karim determine the operating state of the BJT.

Again assume Active Mode.

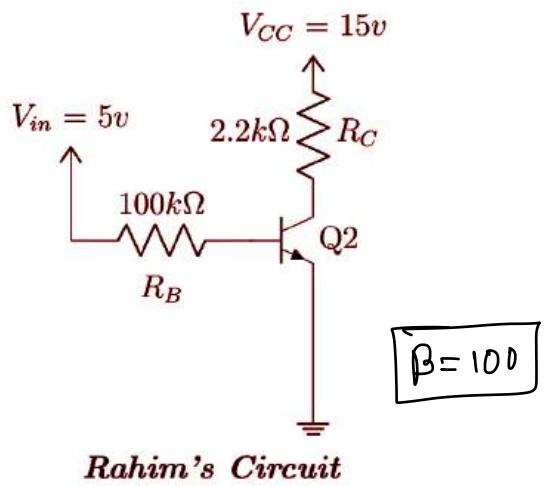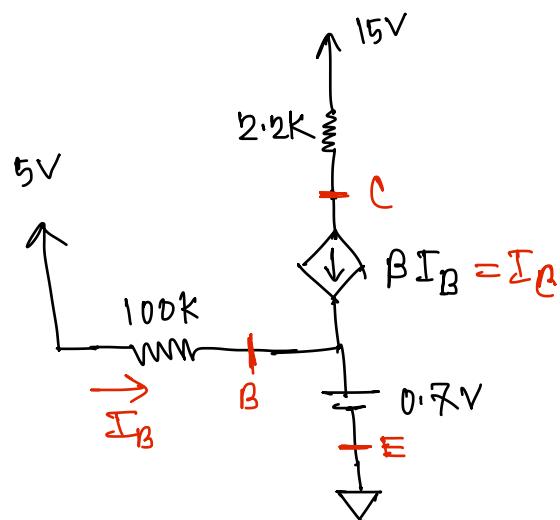

Apply KVL from Base to Emitter,

$$-5 + 100I_B + 0.7 = 0 \quad \text{or, } I_B = 0.043 \text{ mA}$$

$$\text{So, } I_E = \beta I_B = 100 I_B = 4.3 \text{ mA}$$

$$I_E = (\beta + 1) I_B = 101 I_B = 4.343 \text{ mA.}$$

$$V_C = 15 - 2.2 I_C = 5.54 \text{ V}$$

$$V_E = 0 \text{ V}$$

$$\text{So, } V_{CE} = V_C - V_E = 5.54 \text{ V}$$

$$\text{※ Verified } V_{CE} = 5.54 > 0.2 \text{ V}$$

verified Active mode.

Analyze 'Circuit-C' and calculate I_B , I_C , I_E , V_{CE} using the method of assumed states. You must validate your assumptions.

Assume Active mode.

Given, $I_B = 0.04 \text{ mA}$

in Active mode,

$$I_C = \beta I_B = 90 I_B = 3.6 \text{ mA}$$

$$I_E = (\beta + 1) I_B = 91 I_B = 3.64 \text{ mA}$$

$$V_C = 5 - 1 \times I_C = 1.4 \text{ V} \quad | \quad \text{So, } V_{CE} = -2.24 < 0.2 \text{ V} \quad X$$

$$V_E = R_E I_E = 3.64 \text{ V} \quad | \quad \text{Not Active Mode}$$

Assume Saturation. Given,

$$V_{CE} = V_{CB} + V_{BE}$$

$$\text{or, } 0.2 = V_{CB} + 0.8 \quad \text{or, } V_{BC} = 0.6 \text{ V}$$

Applying Kmm Collector line to Emitter line.

$$-5 + I_C - 0.6 + 0.8 + I_E + 0 = 0$$

$$\text{or, } [I_C + I_E = 4.8] \quad \text{--- (1)}$$

$$\text{We know, } I_E = I_c + I_B = I_c + 0.04$$

$$\text{So, from eq. (1), } I_c + (I_c + 0.04) = 4.8$$

$$\text{or, } [I_c = 2.38 \text{ mA}]$$

$$\text{So, } I_E = I_c + I_B = [2.42 \text{ mA}]$$

$$V_{CE(\text{sat})} = 0.2 \text{ V}$$


BJT Parameters

$$\beta = 90$$

$$V_{BE(\text{Active})} = 0.7 \text{ V}$$

$$V_{BE(\text{Saturation})} = 0.8 \text{ V}$$

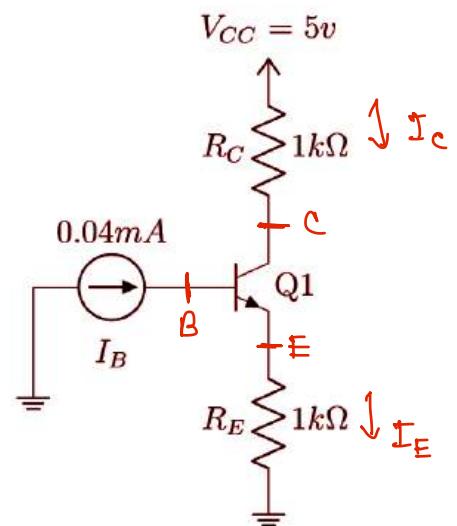
$$V_{CE(\text{Saturation})} = 0.2 \text{ V}$$



Circuit-C

X

Not Active Mode

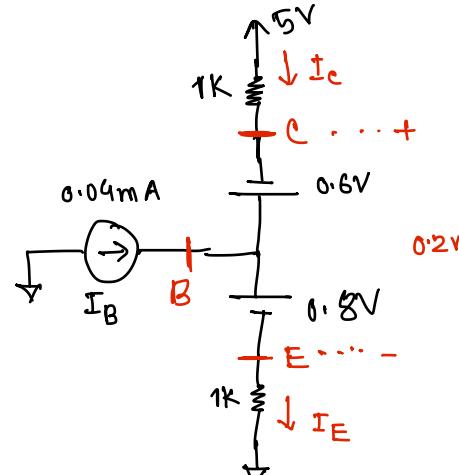

* Verified:

$$\frac{I_c}{I_B} = \frac{2.38}{0.04} = 59.5 < \beta (90)$$

So, verified Saturation.

For 'Circuit-C', the operating state of the BJT found in part-B can be changed by changing the value of V_{CC} . Determine how you should change the value of V_{CC} to change the operating state of the BJT found previously. Show necessary calculation.

Previously Found = Saturation ; where $V_{CE} = 0.2$

Target State = Active ; where $V_{CE} > 0.2$

To change from Saturation to Active, we need to increase V_{CE} .

$$V_{CE} = V_c - V_E = (V_{cc} - I_e R_E) - V_E = V_{cc} - I_c - I_E \quad (\text{from the circuit})$$

So, to increase V_{CE} , we need to increase V_{cc} .

How much should we increase?

Ans: Set $V_{CE} = 0.2$; but solve in Active mode to find V_{cc} .

That value would be the minimum required V_{cc} .

In Active,

$$I_B = 0.04 \text{ mA}, \beta = 50$$

$$I_C = \beta I_B = 3.6 \text{ mA}$$

$$I_E = I_B (\beta + 1) = 3.64 \text{ mA}$$

Applying KVL from V_{cc} to Emitter.

$$-V_{cc} + I_C + V_{CE} + I_E + 0 = 0$$


$$\text{or, } V_{cc} = 3.6 + 3.64 + 0.2$$

$$= 7.44 \text{ V}$$


So, if $V_{cc} > 7.44 \text{ V}$,

only then, V_{CE} would be $> 0.2 \text{ V}$

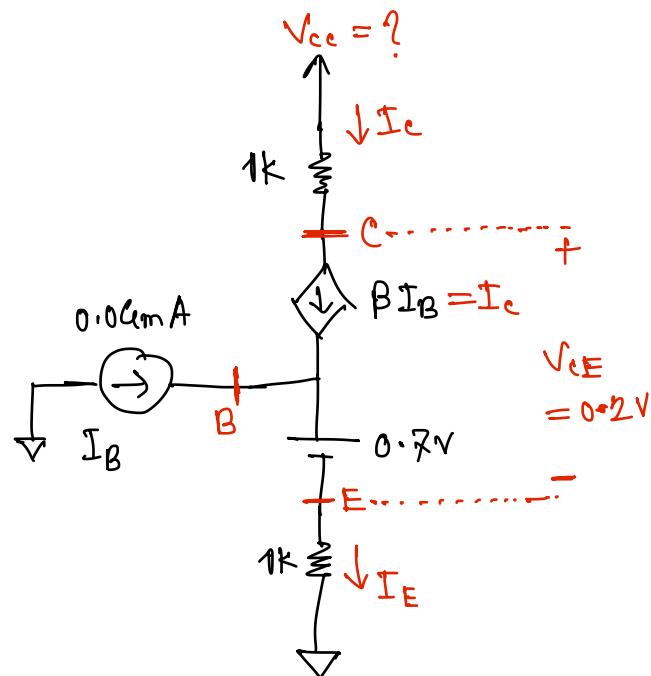We have to set V_{cc} at 7.44 V or higher.



Implement the logic function, $f = \overline{A + BC + D}$ using BJTs where A, B, C, D are boolean inputs.


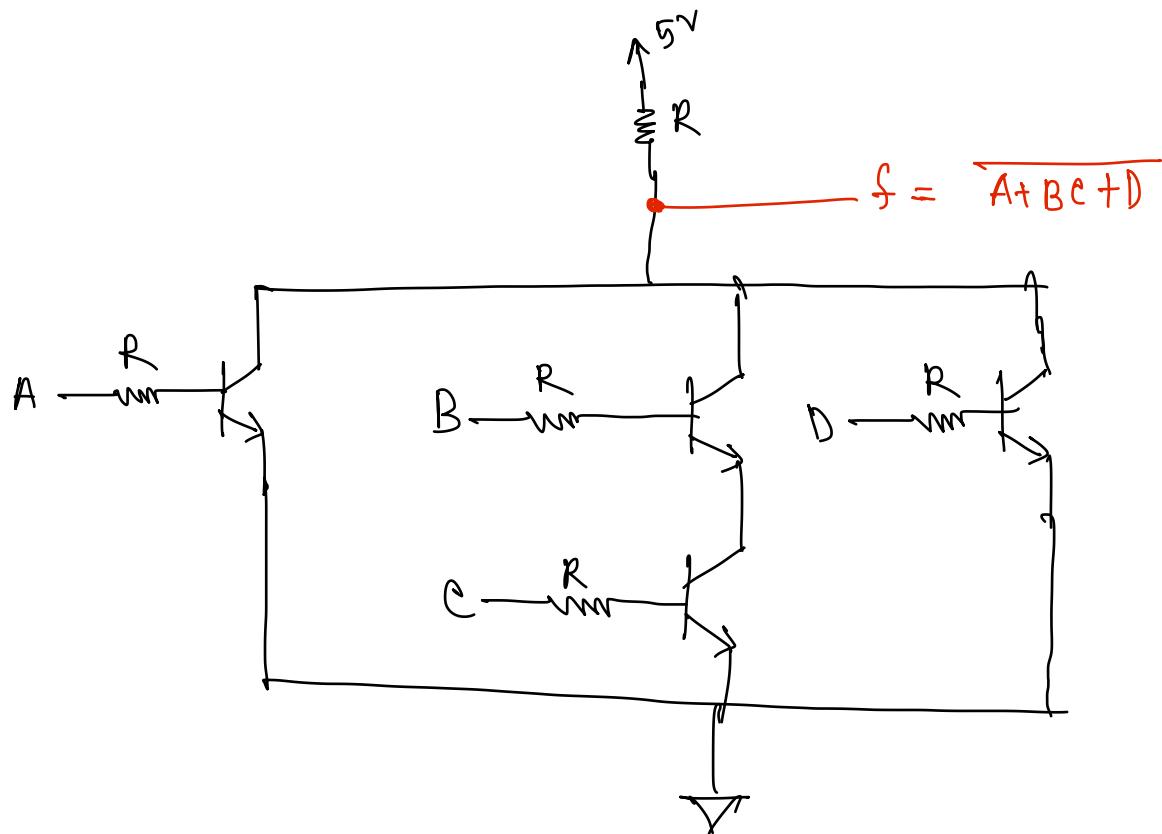


SPRING 2024

Andrew and Nicole found the adjacent circuit built in a trainer board. From the transistor model, they knew it had a gain of $\beta = 80$. They also saw $V_{CC} = 5 \text{ V}$, $R_B = 2 \text{ k}\Omega$, and $R_C = 3 \text{ k}\Omega$. However, the RE resistor was an unknown one. So, they provided an input of $V_{in} = 2 \text{ V}$ and measured the output to be $V_O = 2.2 \text{ V}$. Nicole said, "In this condition, the transistor is in active mode". But, Andrew disagreed.

Design the circuit, i.e., determine the value of R_E , using what Nicole said about the mode of the transistor.

For Active mode, the circuit becomes;

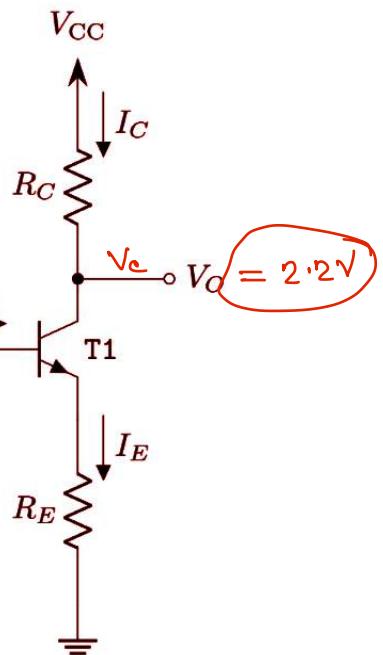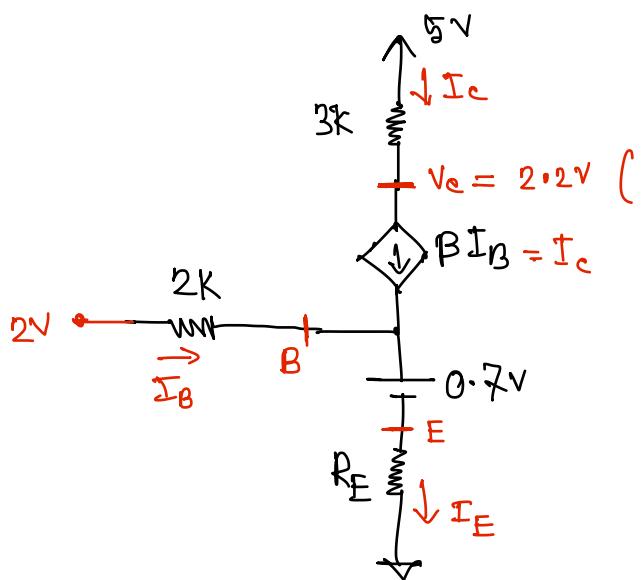

Since, $V_o = V_c = 2.2 \text{ V}$ is given,

$$I_C = \frac{5 - V_c}{3} = \frac{5 - 2.2}{3} = 0.933 \text{ mA}$$

Then, $\beta = 80$ (given) and $I_B = \frac{I_C}{\beta} = 0.0117 \text{ mA}$

Applying KVL across Base to Emitter,

$$-2 + 2I_B + 0.7 + I_E R_E + 0 = 0$$

$$\text{or, } 2I_B + (\beta + 1) I_B R_E = 1.3$$

$$\text{or, } R_E = \frac{1.3 - 2I_B}{(\beta + 1) I_B} = \boxed{1.347 \text{ k}\Omega}$$

Use the previous calculations, and determine who is right between Andrew and Nicole.

$$\text{We got, } R_E = 1.347 \text{ k}\Omega$$

$$\text{So, } V_E = I_E R_E = (\beta + 1) I_B \times 1.347 = (80+1) \times 0.0117 \times 1.347 \\ = 1.276 \text{ V}$$

$$V_C = 2.2 \text{ V} \text{ (Given)} ; \text{ So, } V_{CE} = V_C - V_E = 0.924 \text{ V} > 0.2 \text{ V}$$

So, verified Active mode. So, Nicole was right.

Using the value of R_E obtained previously, determine who will be right if $V_{in} = 4\text{V}$

When, $V_{in} = 4\text{V}$ and $V_{cc} = 5\text{V}$, If should be in Saturation.

I_E Saturation,

KVL along Base \rightarrow Emitter:

$$-4 + 2I_B + 0.8 + 1.34 I_E + 0 = 0$$

KVL along Collector \rightarrow Emitter:

$$-5 + 3I_C + 0.2 + 1.34 I_E + 0 = 0$$

And, we know, $I_C + I_B = I_E$


Solving above eqns, we get,

$$I_B = 0.58 \text{ mA}, \quad I_C = 0.92 \text{ mA}, \quad I_E = 1.511 \text{ mA}$$

* Verify:

$$\frac{I_C}{I_B} = \frac{0.92}{0.58} = 1.586 < \beta (80)$$

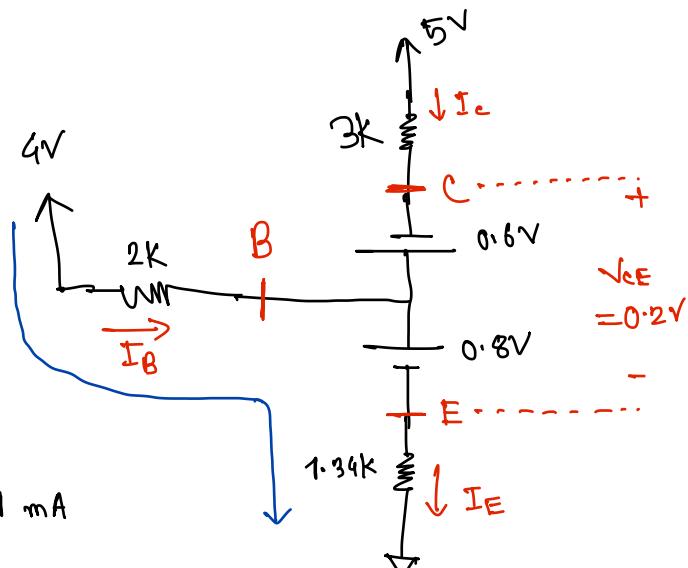So, verified Saturation Mode, this time Andrew would be right.



Find out the currents going through the three terminals of the transistor Q1. Also, determine the value of V_1 and V_2 .

$$\text{Here, } V_1 = V_C$$

$$V_2 = V_E$$

Q1
$\beta = 100$
$v_{CE(\text{Sat})} = 0.2 \text{ V}$
$v_{BE(\text{Act})} = v_{BE(\text{Sat})} = 0.7 \text{ V}$

Assuming Saturation Mode;

Resistor values in ($k\Omega$)				
R_B	R_C	R_E	R_G	R_D
100	1.1	1	3	-

Given,

$$V_{BE(\text{sat})} = 0.7$$

$$V_{CE} = V_{CB} + V_{BE}$$

$$\text{or, } 0.2 = V_{CB} + 0.7 \quad \text{or, } V_{CB} = 0.5 \text{ V}$$

KVL along Base \rightarrow Emitter.

$$-5.5 + 100I_B + 0.7 + I_E + 0 = 0$$

KVL along Collector \rightarrow Emitter

$$-5 + 1.1I_C + 0.2 + I_E + 0 = 0$$

$$\text{We know, } I_B + I_C = I_E$$

$$\text{Solving, } I_B = 0.025 \text{ mA}$$

$$I_C = 2.273 \text{ mA}$$

$$I_E = 2.298 \text{ mA}$$

$$V_C = V_1 = 5 - 1.1I_C = 2.5 \text{ V}$$

$$V_2 = V_E = I_E R_E = 2.298 \text{ V}$$

$$\underline{\text{Verify:}} \quad \frac{I_C}{I_B} = \frac{2.273}{0.025} = 90.92 < \beta (100)$$

So, verified Saturation Mode.

