

ASSIGNMENT-4

Full Marks: 50

Q1. [CO1]

10

a) **Show** the IV characteristics graph of both MOSFET and BJT. Identify the different operating regions in the graphs.

b) **Draw** the VTC of a NOR gate using MOSFET S model.

Q2. [CO3]

10

Design a circuit using both MOSFETs and BJTs to implement the following expressions.

a) $f = \overline{(\bar{A} + B)} \cdot C$

b) $f = \overline{(A + B)} + A + CD$


Q3. [CO2]

10

For the transistor $\beta = 100$,

$V_{BE, Active} = 0.7V$, $V_{BE, Sat} = 0.8V$ and

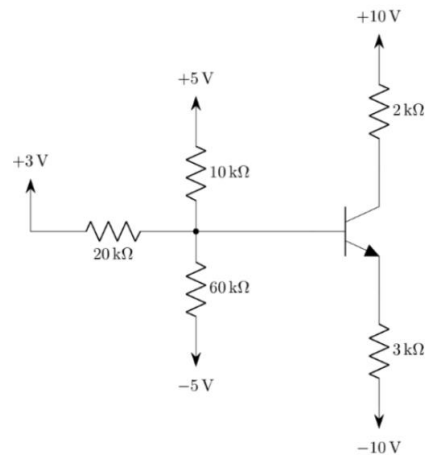
$V_{CE, Sat} = 0.2V$. Determine the operating region of the transistor.



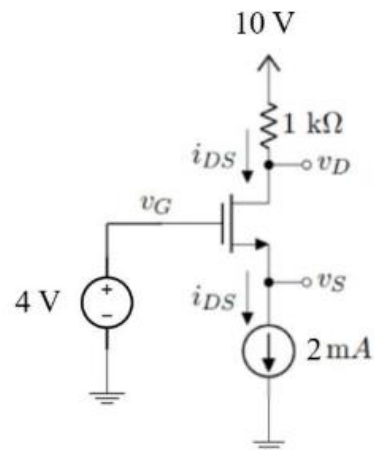Q4. [CO2]

10

Analyze the circuit to find V_D , use method of assume state. You must validate your assumptions. For the MOSFET, $V_T = 1V$ and $k = 4mA/V^2$.



Q5. [CO2]

10

Calculate the value of V_{OUT} , I_{RD1} and I_{RD2} using the method of assumed state. You must validate your assumptions.

