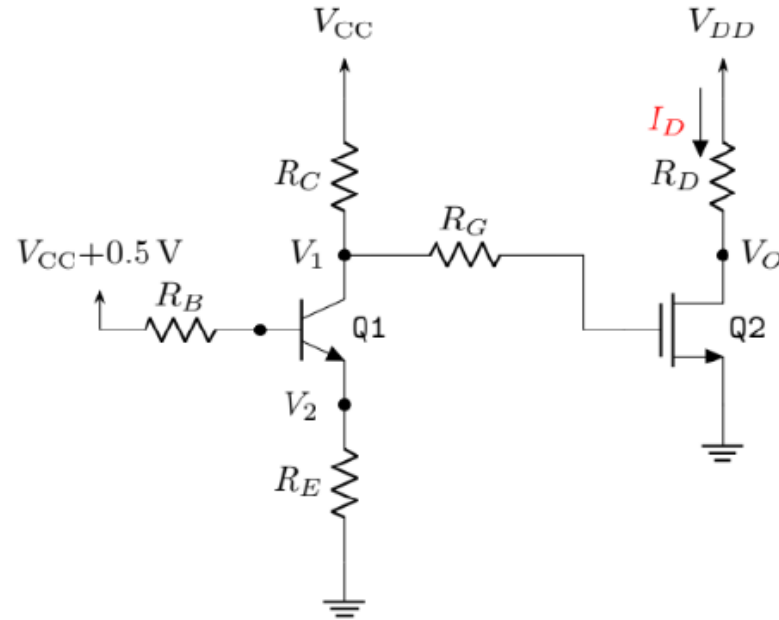


Problem-1

Answer the questions (a-d) based on the circuit shown below. the parameter values of the circuit are given in the adjacent table:



Resistor values in ($k\Omega$)					Supply Voltages	
R_B	R_C	R_E	R_G	R_D	$V_{CC} = 5\text{ V}$	
100	1.1	1	3	-	$V_{DD} = 10\text{ V}$	

Transistor Parameters

Q1	Q2
$\beta = 100$	$k'_n = 0.25\text{ mA/V}^2$
$v_{CE(\text{Sat})} = 0.2\text{ V}$	$W/L = \frac{0.72\text{ }\mu\text{m}}{0.18\text{ }\mu\text{m}}$
$v_{BE(\text{Act})} = v_{BE(\text{Sat})} = 0.7\text{ V}$	$V_T = 1\text{ V}$


Active	Saturation
$I_B = 0.024$	$I_B = 0.025$
$I_C = 2.4$	$I_C = 2.273$
$I_E = 2.424$	$I_E = 2.3$
$V_{CE} = -0.064$	$V_{CE} = 0.2\text{ v}$
	$V_1 = V_C = 2.5$
	$V_2 = 2.3$

Based on the above scenario, answer the following questions:

- [CO1] In the Switch Model of BJT, **Determine** in which mode does a BJT operate when it is OFF? [2]
Which mode does it operate in when it is ON?
- [CO2] **Find out** the currents going through the three terminals of the transistor Q1. [4]
- [CO2] **Determine** the the value of V_1 and V_2 . [1]
- [CO3] **Design** the circuit, i.e. find an appropriate value of R_D , such that Q2 remains at the edge of [3]
saturation, i.e., when $V_{DS} = V_{GS} - V_T$.

$I_D = 1.125$
 $R_D = 7.5k$


Problem-2

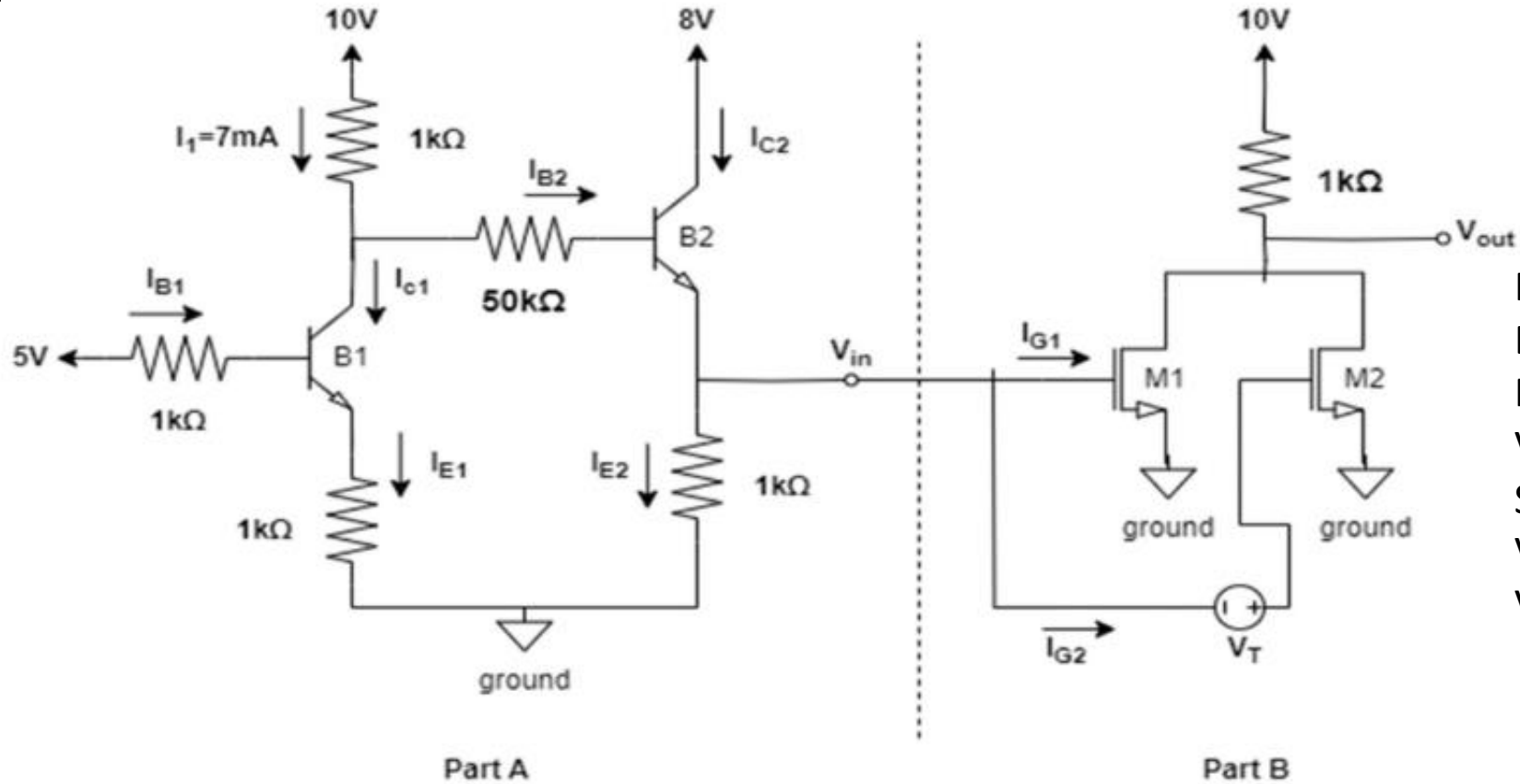

For BJTs
 $B=100$
 Forward Active:
 $V_{BE} = 0.7\text{ V}$
 Saturation:
 $V_{BE} = 0.8\text{ V}$
 $V_{CE} = 0.2\text{ V}$

- Determine i_{g1} and i_{g2} .
- Assume B_1 and B_2 are in the saturation region. Calculate i_{C2} .
- Assume B_1 is in the forward active region. Calculate V_{in} .
- Draw the VTC of part-B assuming $V_T = 8\text{ V}$. [Use S model of MOSFETs]

Problem-3

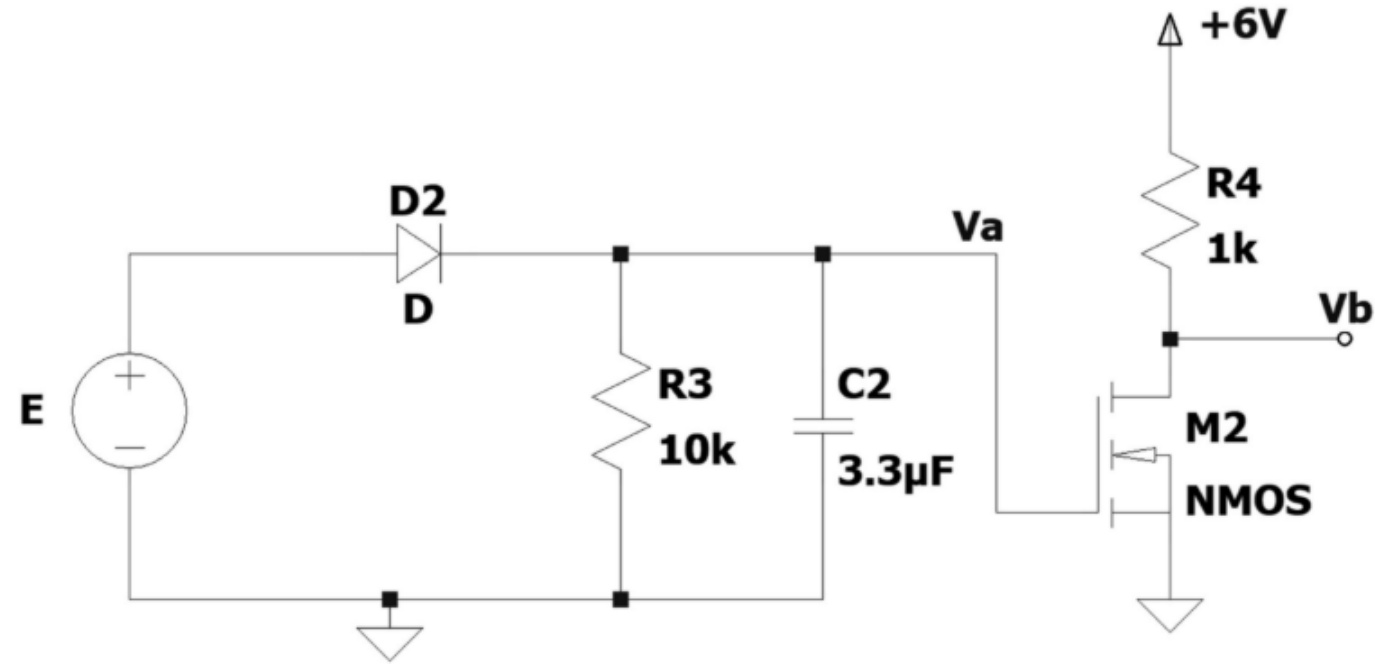


The Half-wave rectifier circuit has been cascaded with an inverter. You are given the following information about the circuit: [For HW: $V_o = V_{dc} \pm V_{ripple}/2$]

$E = 6 \sin(400\pi t) V$	$K_n = 2 mA/V^2$	$V_T = 1 V$	$V_{Do} = 0.7 V$
--------------------------	------------------	-------------	------------------

- Determine** the peak-to-peak ripple value of the half-wave rectifier output, V_a . What is the lowest value of V_a ? [3+1]
- At the lowest value of V_a , **determine** the output V_b of the inverter. [4]
- Now disconnect the capacitor. In this case, **find out** the voltage V_b for the lowest value of V_a . [2]

Problem-4

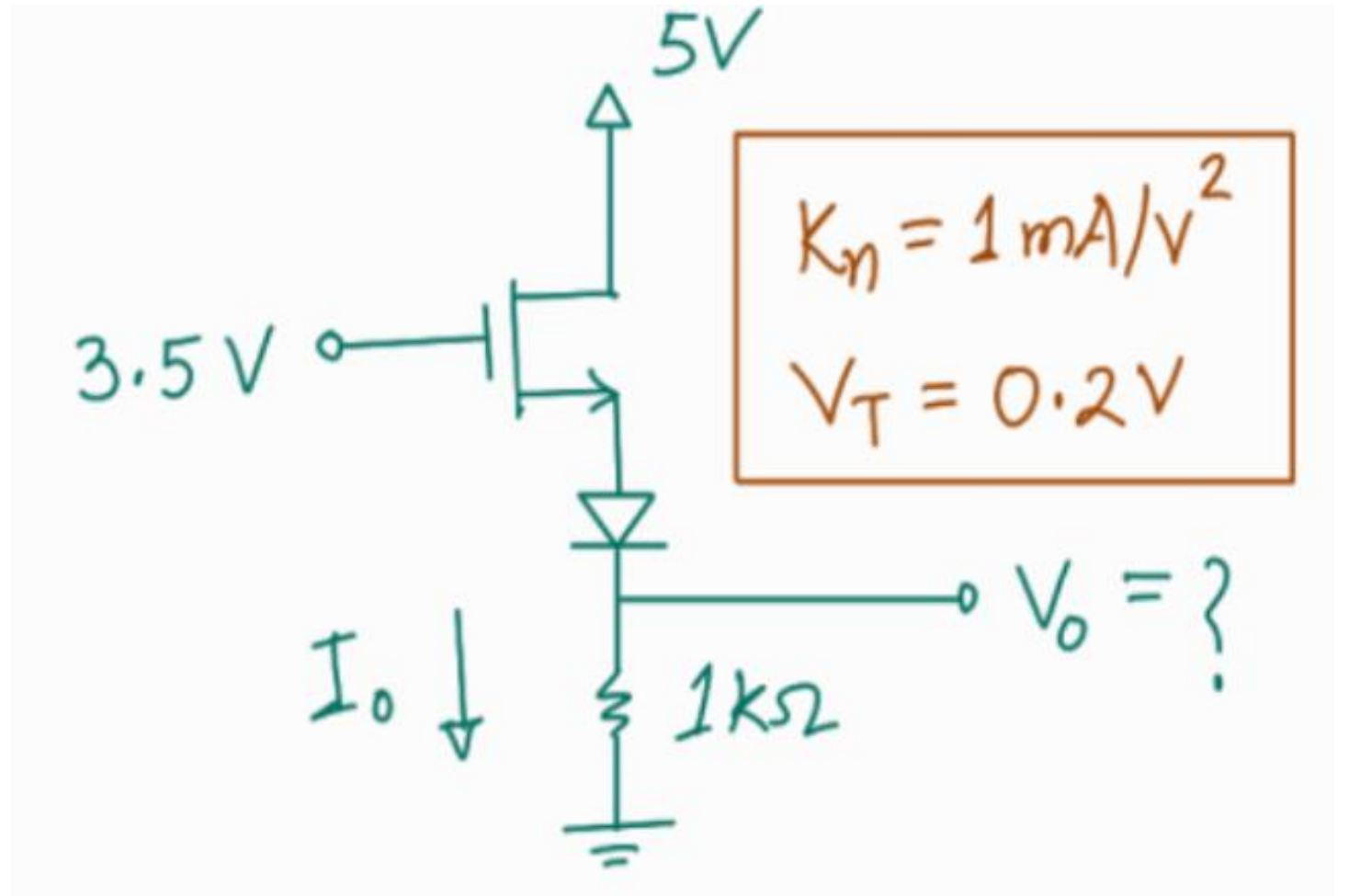

Problem-5

$$K_n = 5 \text{ mA/V}^2$$

$$V_T = 1 \text{ V}$$

Answer the following questions for **Figure-1** where $R_1 = 1\text{k}\Omega$, $R_2 = 2\text{k}\Omega$, $R_3 = 3\text{k}\Omega$, $R_4 = 4\text{k}\Omega$.

- Why a MOSFET can be used as a switch? **Explain** briefly.
- Analyze** the circuit in *Figure-1* to **determine** the values of I_C , I_B , I_E , v_C of T_1 .
- Analyze** the circuit in *Figure-1* to **determine** the value of I_{DS_2} , v_O of T_2 .

Bonus: **Design** a circuit with the boolean inputs A, B, C, D using ideal MOSFETs (S-model) implement the logic function, $f = \overline{A.C} + B.D$

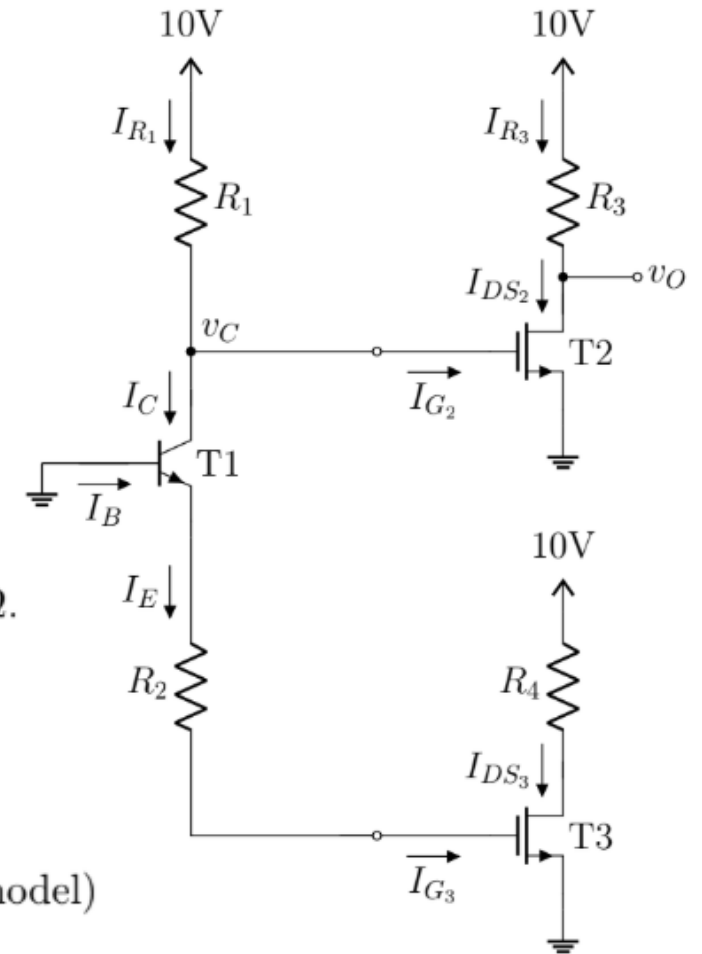


Figure-1