

CSE 251 Assignment [Solution]


1)

$$a) \frac{V_{in} - (-4)}{-4} = \frac{V_o - 8}{8+4}$$

$$V_o = -3V_{in} - 4$$


$$V_s^+ = 8V$$

$$V_s^- = -8V$$

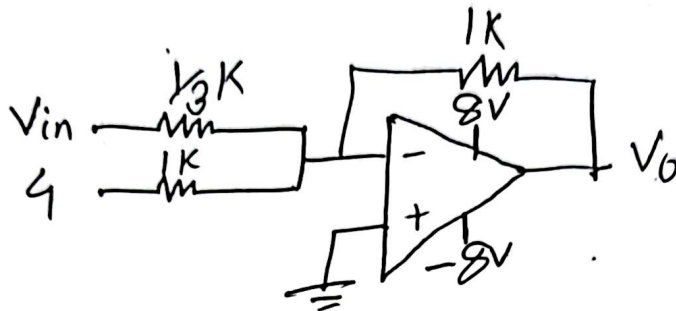

b)

$$V_o = -6\sin(\omega t) - 4$$

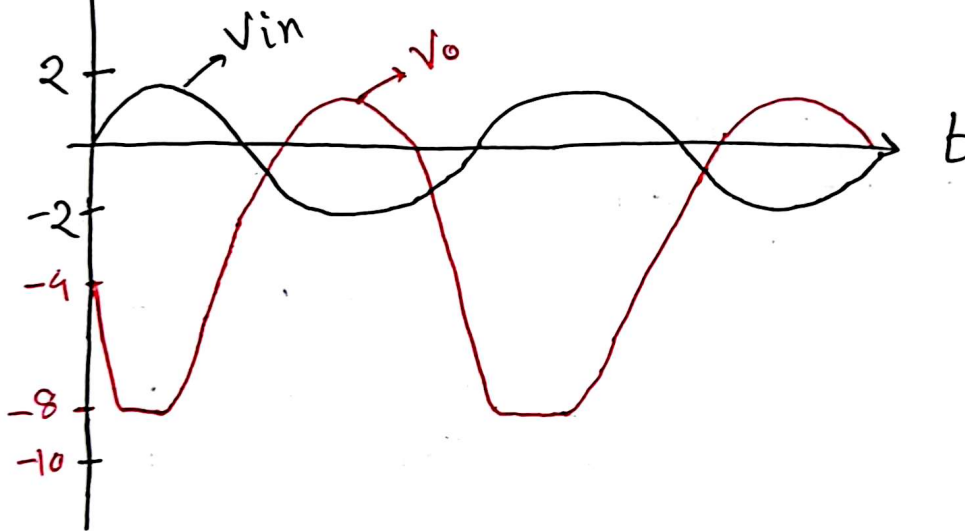

2) a)

KCL at Node V_a

$$\frac{V_a - 5}{2} + \frac{V_a - (-5)}{3} = 0$$

$$\Rightarrow \frac{V_a}{2} + \frac{V_a + 5}{3} = 0$$

$$\Rightarrow 3V_a + 2V_a + 10 = 0$$

$$\Rightarrow 5V_a = -10$$

$$\Rightarrow V_a = -2V$$



$$V_o = \left(1 + \frac{R_f}{R_i}\right) V_{in}$$

$$\Rightarrow -4 = \left(1 + \frac{R_f}{R_i}\right) \times (-2)$$

$$\Rightarrow 2 = \left(1 + \frac{R_f}{R_i}\right)$$

$$\Rightarrow 1 = \frac{R_f}{R_i}$$
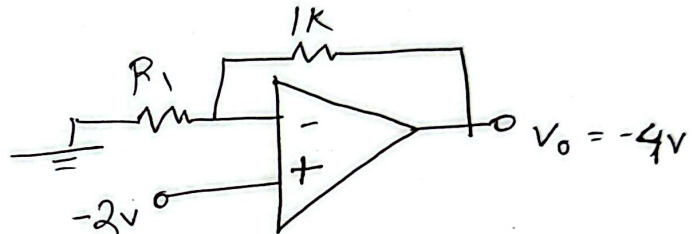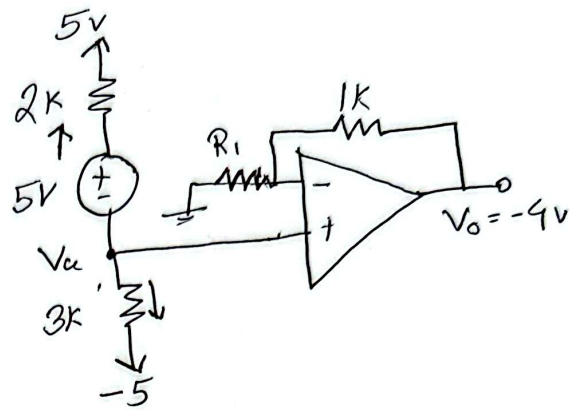
$$\Rightarrow R_i = 1K\Omega \quad [\because R_f = 1K\Omega]$$



Non-Inverting Amplifier

2) b)

KCL at Node V_1

$$\frac{V_1 - 9}{4} + \frac{V_1 - V_0}{8} + \frac{V_1 - 4}{4} = 0$$

$$\Rightarrow 2V_1 - 18 + V_1 - V_0 + 2V_1 - 8 = 0$$

$$\Rightarrow 5V_1 - V_0 = 26 \quad \text{--- (i)}$$

KCL at Node $4V$

$$\frac{4 - V_1}{4} + \frac{4 - V_0}{2} = 0$$


$$\Rightarrow 4 - V_1 + 8 - 2V_0 = 0$$

$$\Rightarrow V_1 + 2V_0 = 12 \quad \text{--- (ii)}$$

Solving eqn (i) & (ii)

$$V_1 = 5.82V$$

$$V_0 = 3.09V$$

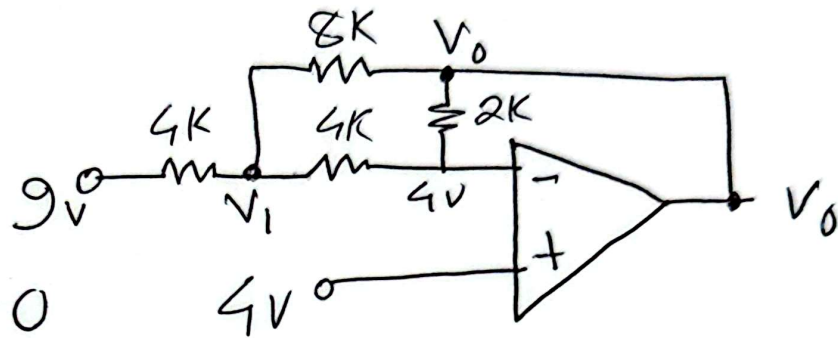


3) a) Assuming $D \rightarrow OFF$

$$V_{D0} = 0.6$$

$$V_A = \frac{2}{2+2} \times 5 = 2.5V$$

$$V_C = \frac{2}{2+3} \times 5 = 2V$$
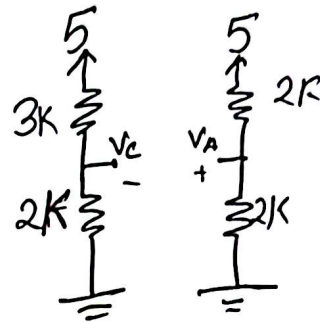
$$V_D = V_A - V_C = 2.5 - 2 = 0.5 < V_{D0}$$



Correct Assumption

$$i_D = 0$$

$$V_D = 0.5V$$

b) Assuming $D \rightarrow ON$

$$V_1 \left(\frac{1}{2} + \frac{1}{3} \right) + V_2 \left(\frac{1}{2} + \frac{1}{2} \right) - \frac{5}{3} - \frac{5}{2} = 0$$


(i)

$$V_2 - V_1 = 0.3$$

Solving eqn

$$V_1 = 2.1V$$

$$V_2 = 2.4V$$

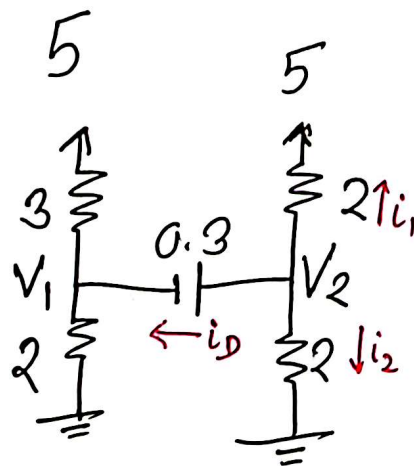

KVL at V_2

$$\hat{i}_1 = \frac{2.4 - 5}{2} = -1.3$$

$$\hat{i}_1 + i_2 + i_D = 0$$

$$i_2 = \frac{2.4 - 0}{2} = 1.2$$

$$\Rightarrow i_D = -\hat{i}_1 - i_2$$

$$= -(-1.3) - 1.2 = 0.1 \text{ mA} > 0$$

Assumption is correct

$$\boxed{\begin{array}{l} I_D = 0.1 \\ V_D = 0.3 \end{array}}$$

4)

a) $R = 100 \text{ k}$

Assuming D_1 & D_2 ON

KVL at L_1

$$0 = -0.7 + 0.7 + 100 I_{D_2} - 2$$

$$\Rightarrow I_{D_2} = \frac{2}{100} = 0.02 \text{ mA} > 0$$


KCL at V_n

$$5 = i_{D_1} + i_{D_2}$$

$$\Rightarrow i_{D_1} = 5 - 0.02 = 4.98 \text{ mA} > 0$$

Correct assumption
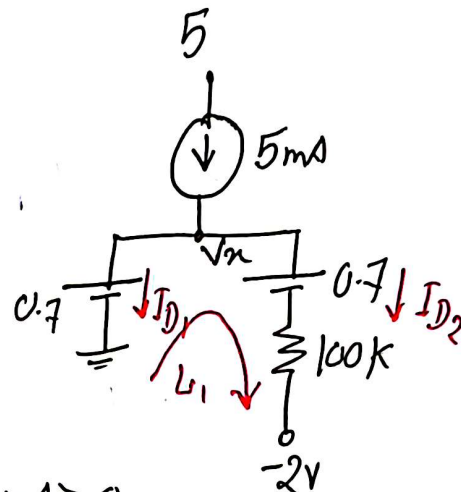
$$\boxed{\begin{array}{l} i_{D_2} = 0.02 \text{ mA} \\ i_{D_1} = 4.98 \text{ mA} \end{array}}$$



b) $R = 0.02K$

Assuming D_1 & D_2 ON

$$0 = -0.7 + 0.7 + 0.02 i_{D2} - 2$$

$$\Rightarrow i_{D2} = 100mA$$

$$5 = i_{D1} + i_{D2}$$

$$\Rightarrow i_{D1} = -95mA \neq 0 \quad \text{invalid assumption}$$

Assuming D_1 OFF, D_2 ON

$$i_{D2} = 5mA > 0$$

$$V_n = 0.7 + 0.02 i_{D2} - 2$$



$$= -1.2$$

$$V_{D1} = V_n - 0 = -1.2 < 0.7$$

assumption is correct

$$i_{D1} = 0mA$$


$$i_{D2} = 5mA$$

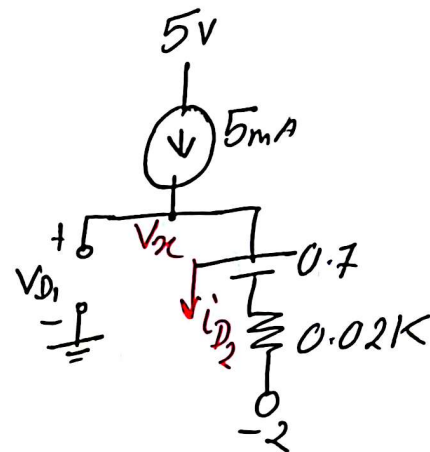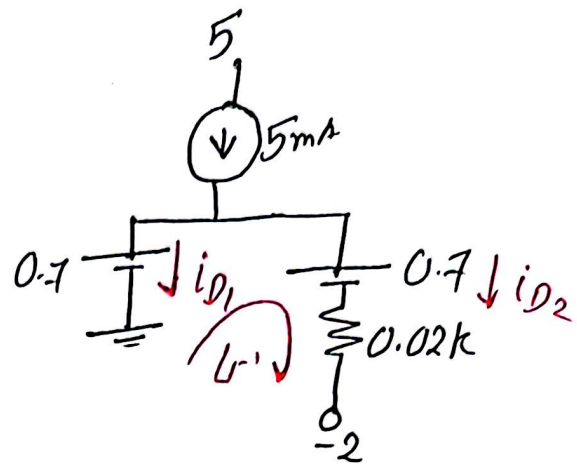

6)

a) Assuming D_1 ON

KCL at Super Node

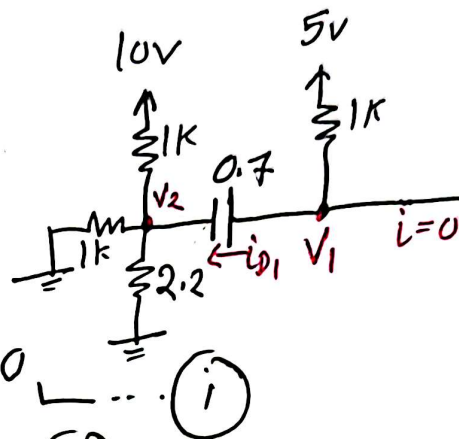

$$\frac{V_1 - 5}{1} + \frac{V_2 - 10}{1} + \frac{V_2}{2.2} = 0 \quad \text{--- (i)}$$

$$V_1 - V_2 = 0.7 \quad \text{--- (ii)}$$

Solving eqn (i) & (ii)

$$V_1 = 4.84$$

$$V_2 = 4.14$$

$$i_{D1} = \frac{5 - 4.84}{1} = 0.16 \text{ mA} > 0$$

$D_1 \rightarrow$ Forward bias


Assumption is correct

b) $V_a = V_1 = 4.84 \text{ V}$



$$V_o = \left(1 + \frac{1.8}{1.2}\right) \times 4.84$$

$$= 12.1 > 10$$

$\therefore V_o = 10 \text{ V}$

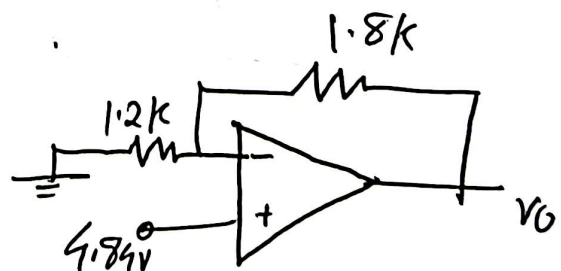


7) Ideal Model

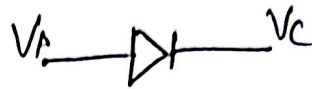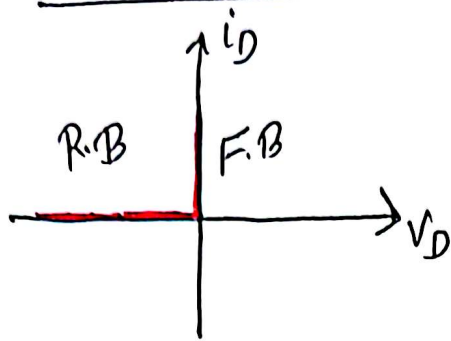

F.B \longrightarrow \Rightarrow Short Circuit

R.B \longrightarrow \Rightarrow Open Circuit


CVD Model

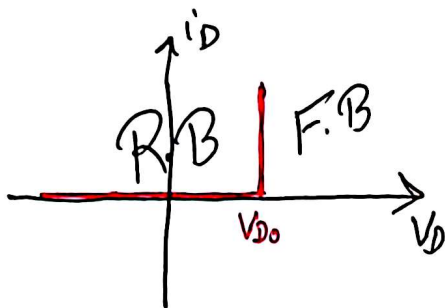

F.B $V_A + V_{D0} - V_C$

R.B \longrightarrow \longrightarrow

CVD + R Model

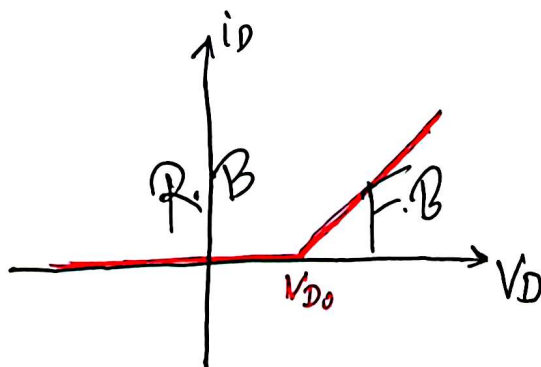

F.B $V_A + V_{D0} - V_C - i_D r_{cd}$

R.B \longrightarrow \longrightarrow